
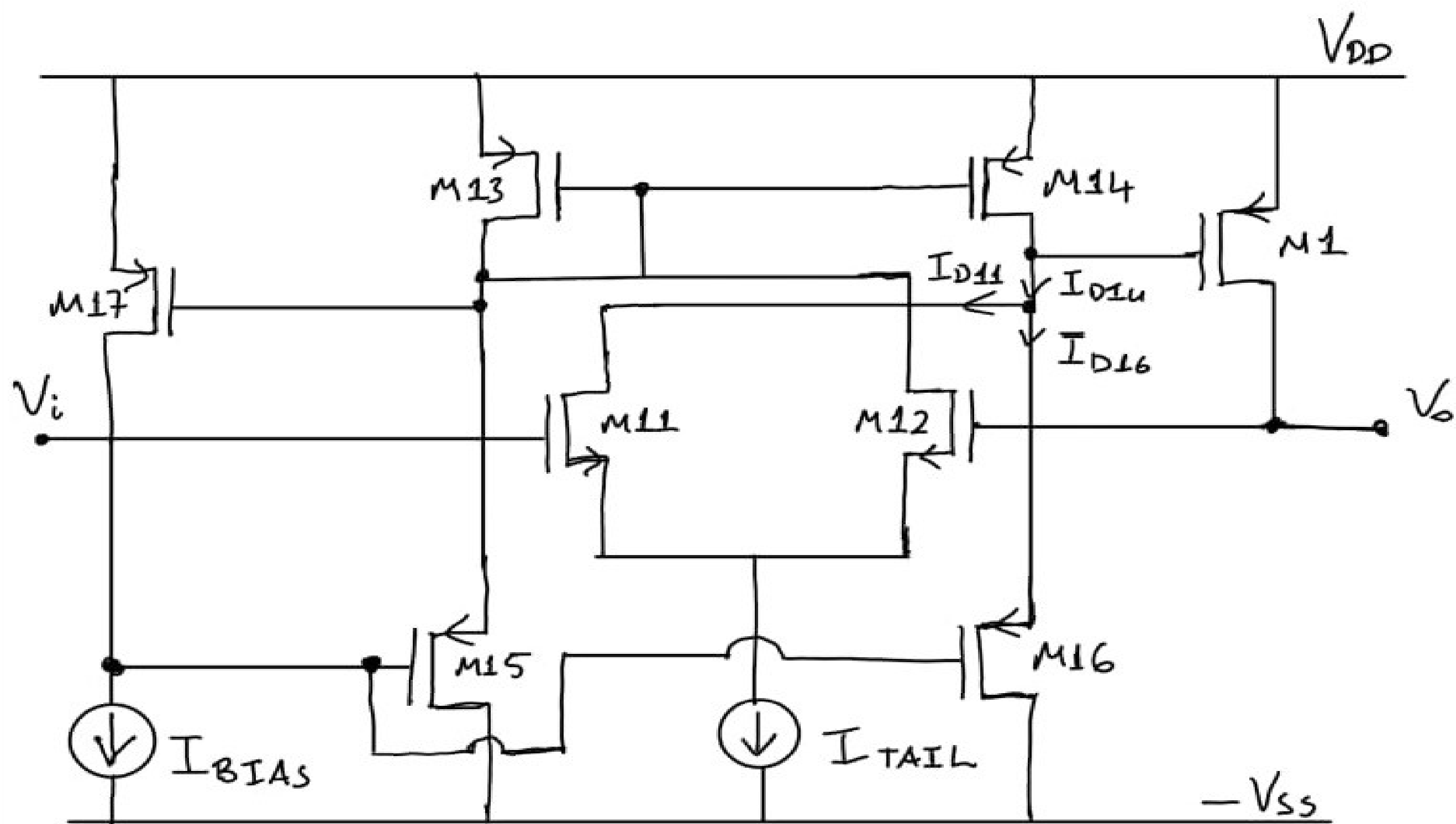


# HW10

ARDA ÜNAL

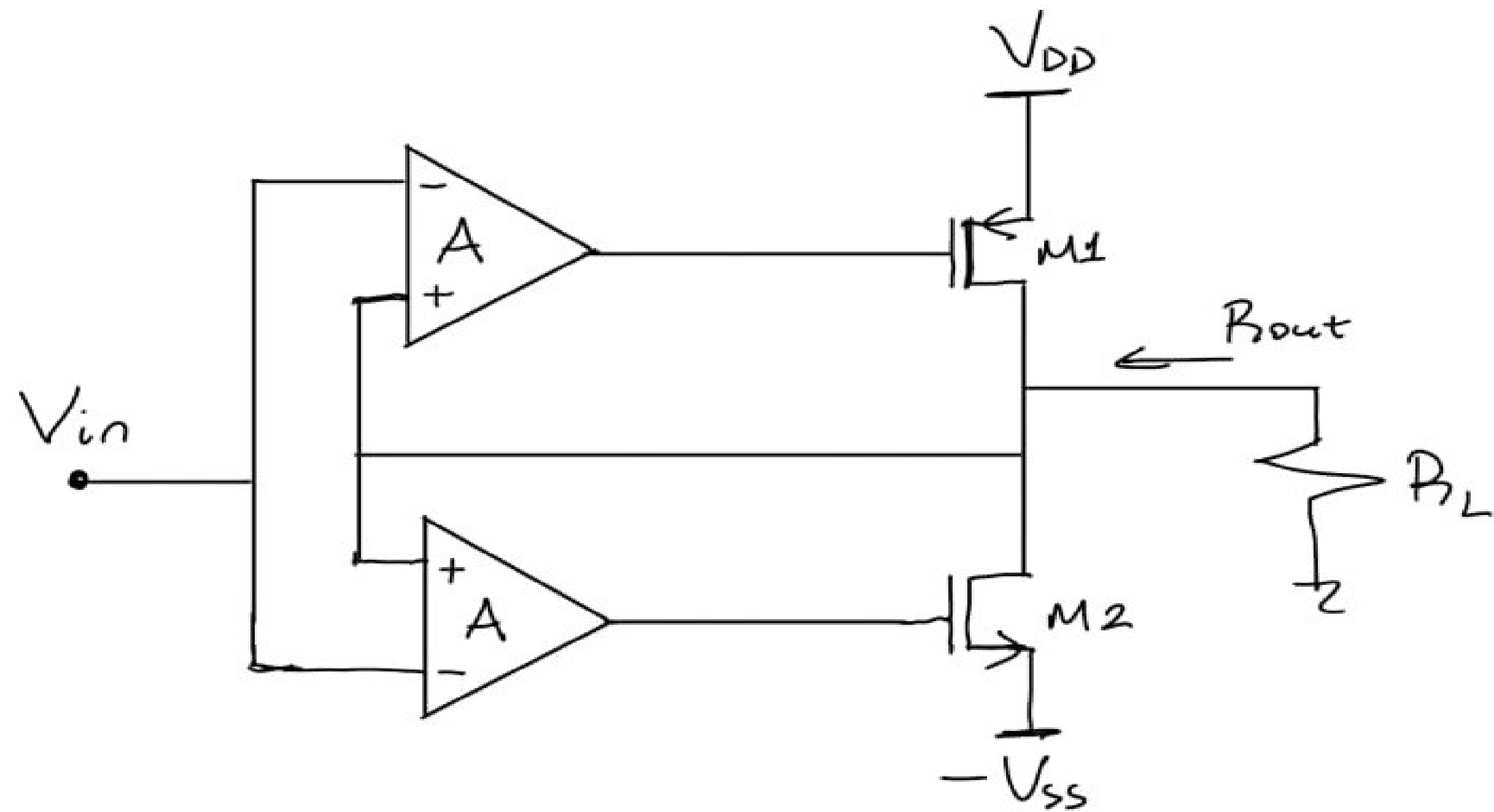

$$A = \frac{g_{m11}}{g_{m16} + g_{m14}}$$

→ Our aim is to find an appropriate value of gain  $A$ .

$2A g_m R_L \gg 1$ , since  $R_L = 100 \Omega$   
 $\Rightarrow A g_m \gg 5 \times 10^{-3}$ , Let  $V_{DD} - V_{SS} = 3V$ , then

$$I_D^{\max} = \frac{1.5}{100} = 15 \mu A, \text{ since } V_{TN} = 0.8V$$

$$g_m = \frac{2I_D^{\max}}{0.7} \Rightarrow g_m = 42.8 \text{ mS}$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 488.49 \Rightarrow \begin{matrix} L_1 = 0.15 \mu m \\ W_1 = 73.27 \end{matrix}$$

$$\Rightarrow A \gg 0.1168 \Rightarrow \text{Let us choose } A = 1 \text{ then}$$

$$\Rightarrow A = \frac{g_{m11}}{g_{m16} + g_{mb16}} \Rightarrow \begin{matrix} g_{mb16} = 0.35 g_{m16} \\ \text{for } n = 1.35 \end{matrix}$$

$$\Rightarrow A = \frac{g_{m11}}{1.35 g_{m16}} \Rightarrow \frac{g_{m11}}{g_{m16}} = 1.35$$

$$\rightarrow \text{Thus let } g_{m11} = 1.35 \text{ mS and } g_{m16} = 1 \text{ mS}$$

$$\Rightarrow I_{D16} = 100 \mu A \text{ and } I_{D11} = 135 \mu A$$

$$\Rightarrow I_{D14} = I_{D16} + I_{D11} = 235 \mu A$$

$$\left(\frac{W}{L}\right)_{14} = \frac{g_{m14}^2}{2k' I_D} = 94, \left(\frac{W}{L}\right)_{11} = 22.5$$


$$\left(\frac{W}{L}\right)_{16} = 16.667, I_{TAIL} = 270 \mu A$$

$$\Rightarrow I_{D1} = I_{BIAS} \frac{(W/L)_2}{(W/L)_{17}} \Rightarrow \frac{I_{BIAS}}{(W/L)_{17}} = 3.07 \times 10^{-5}$$

$$\Rightarrow \text{For } I_{BIAS} = 100 \mu A, \left(\frac{W}{L}\right)_{17} = 3.25$$

$$\left(\frac{W}{L}\right)_2 = \frac{0.625}{1.5} \left(\frac{W}{L}\right)_1 = 203.5$$
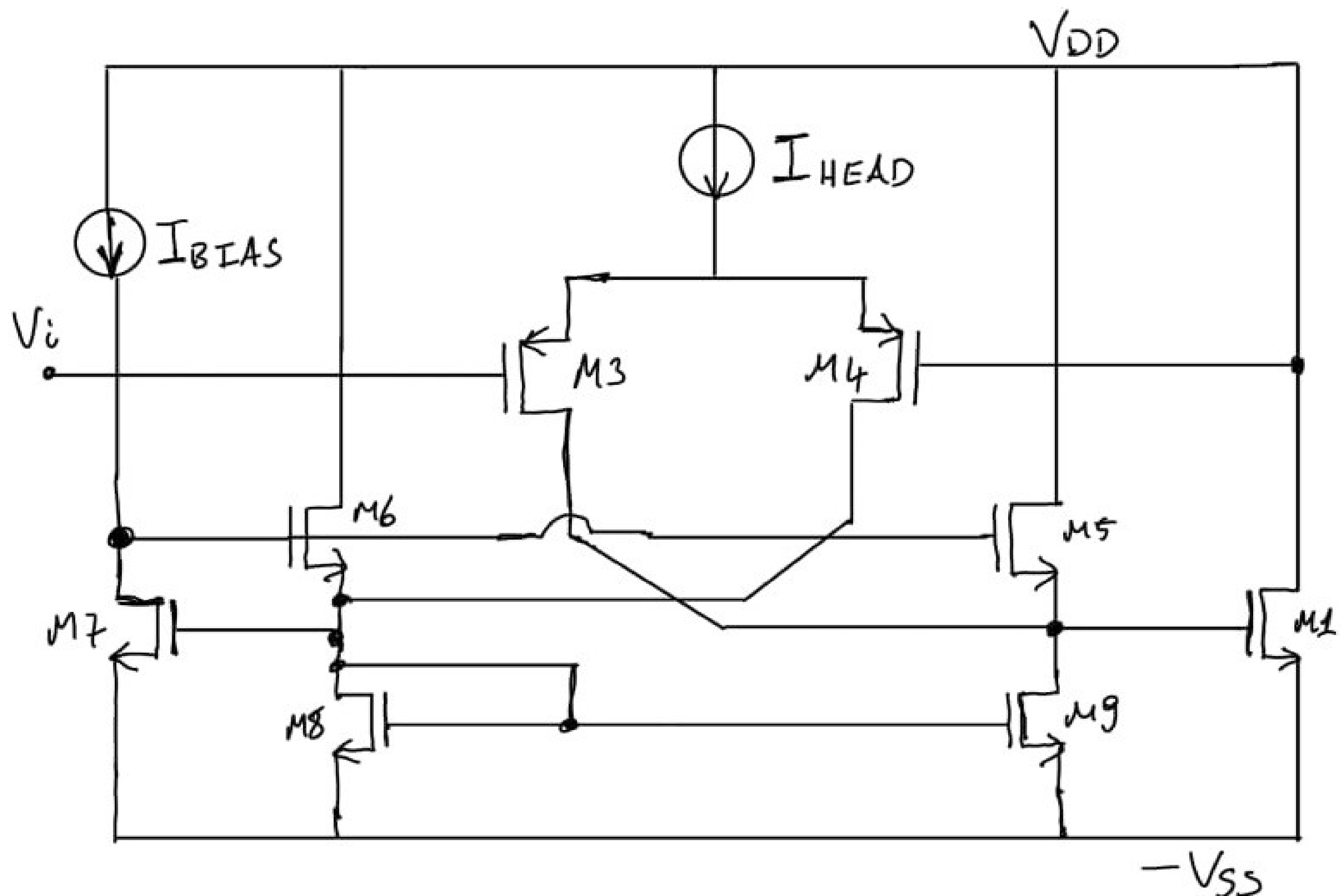
$$\Rightarrow L_1 = 0.5 \mu m, W_1 = 30.5 \mu m$$



$$I_3 + I_5 = I_9 \quad I_3 = \frac{I_{HEAD}}{2}$$

$$A = \frac{g_{m3}}{g_{m5} + g_{m65}} = 1 \Rightarrow \text{Again } g_{m5} + g_{m65} = 1.35 g_{m5}$$

$$\rightarrow \text{Let } g_{m3} = 1.35 mS$$

$$\Rightarrow \frac{g_{m3}}{g_{m5}} = 1.35 \Rightarrow g_{m5} = 1 mS$$

$$\Rightarrow I_{D3} = 135 \mu A \text{ and } I_{D5} = 100 \mu A$$

$$\Rightarrow I_9 = 235 \mu A, I_{HEAD} = 270 \mu A$$


$$\Rightarrow \left(\frac{W}{L}\right)_{3,4} = 54, \left(\frac{W}{L}\right)_{5,6} = 16.667$$

$$\Rightarrow \left(\frac{W}{L}\right)_{8,9} = 39.1667$$

$$I_{D1} = I_{BIAS} \frac{(W/L)_1}{(W/L)_7} \Rightarrow \frac{I_{BIAS}}{(W/L)_7} = 7.37 \times 10^{-5}$$


$$\text{For } I_{BIAS} = 100 \mu A \quad (W/L)_7 = 1.35$$

# Upper side of the circuit

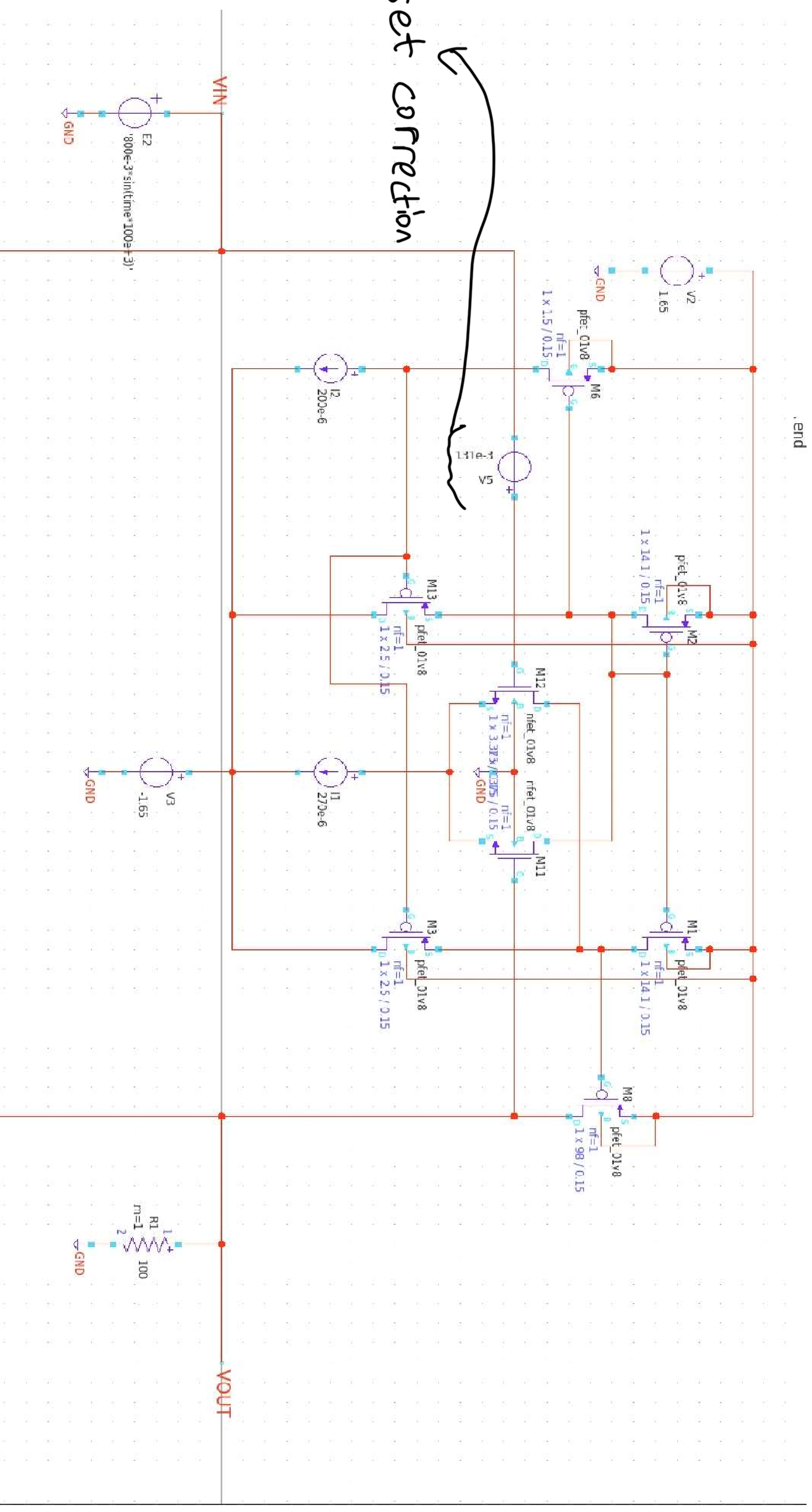

→ I did some corrections by playing  $I_{BIAS}$ ,  $W_{M6}$ , and  $W_{M8}$ . Addition to that I added voltage source  $V_5$  to remove the offset.

Below side of the circuit

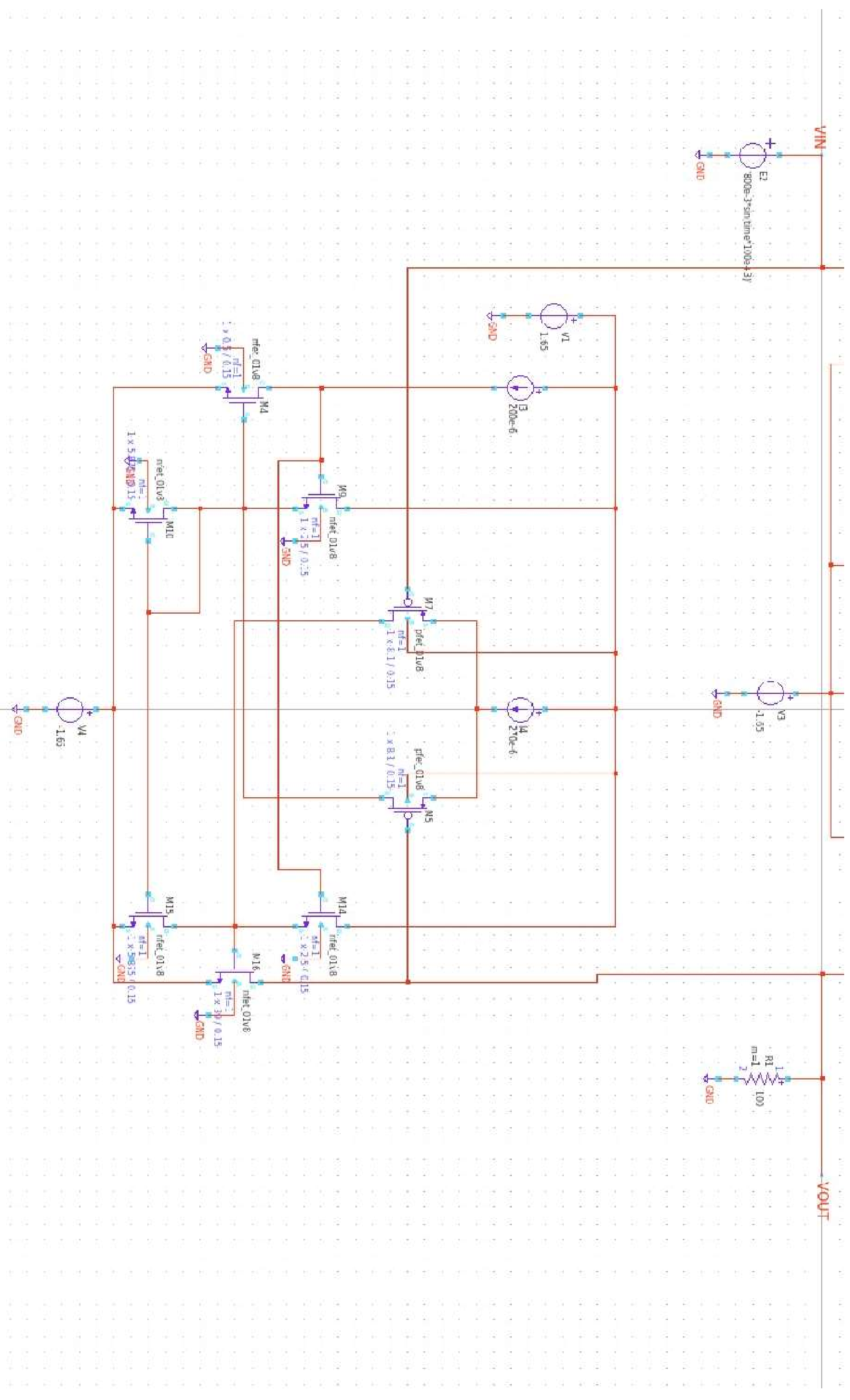


→ I also did some corrections here by changing  $I_{B1A5}$

$W_{M4}$  and  $W_{M16}$




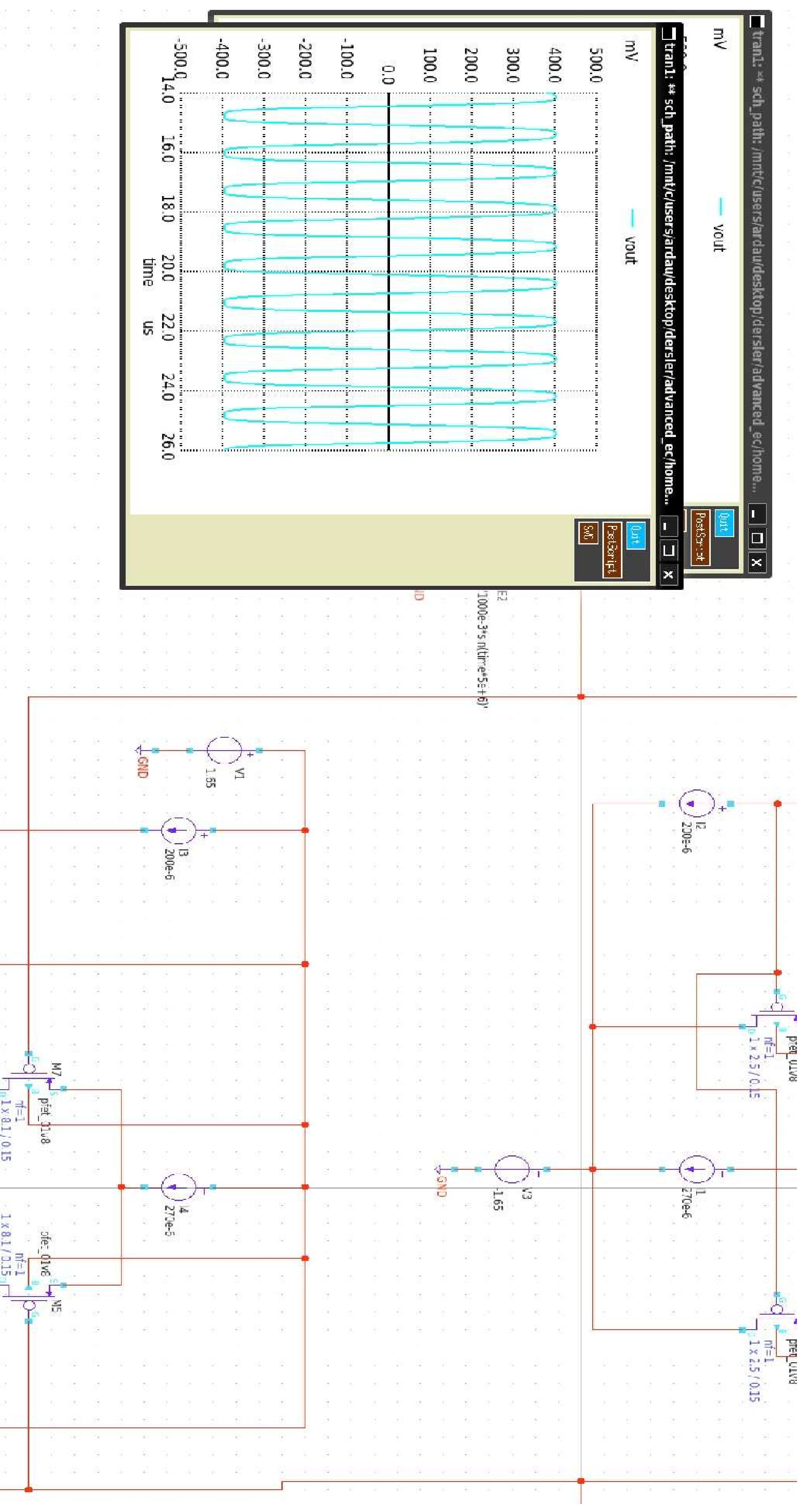→ This is the maximum output that is available for this circuit.






$$f_{vin} = 1 \text{ kHz}$$

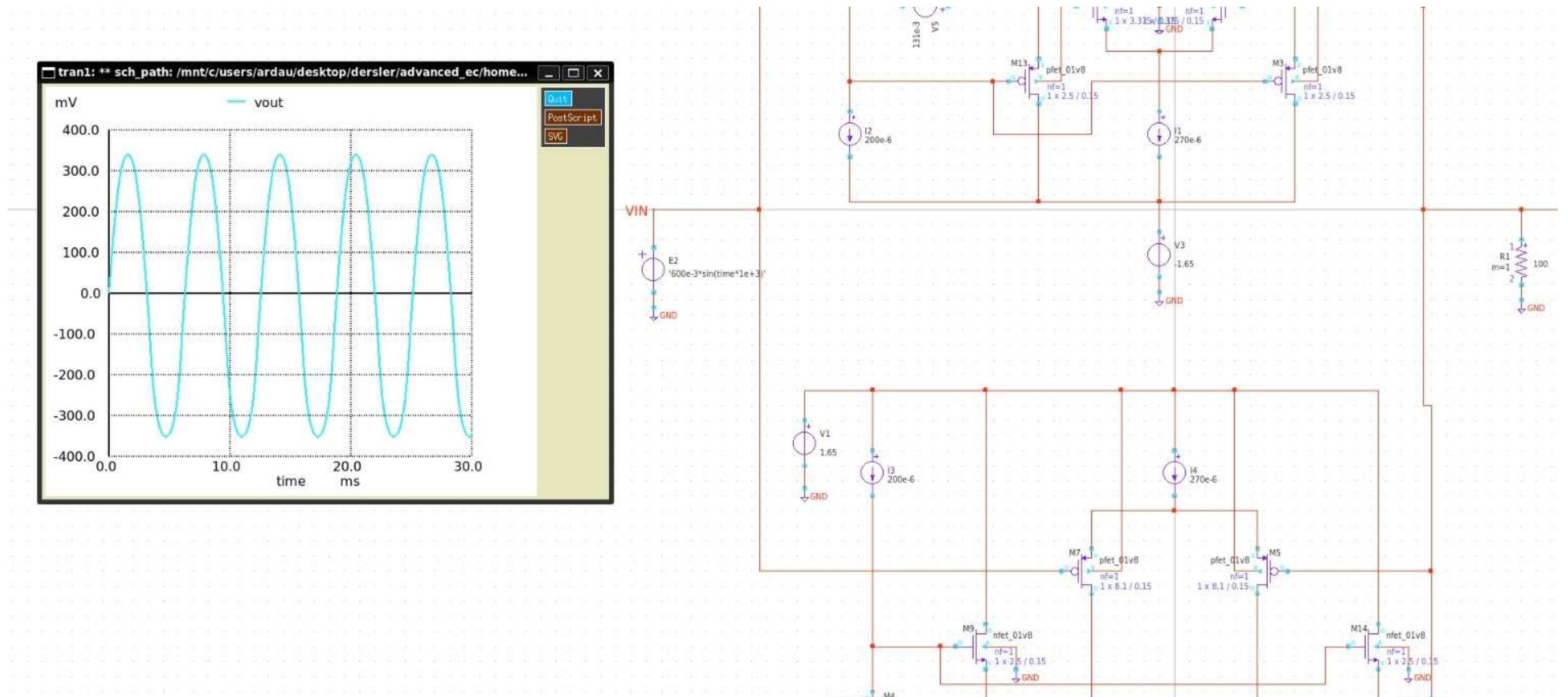


$$f_{vin} = 10 \text{ kHz}$$

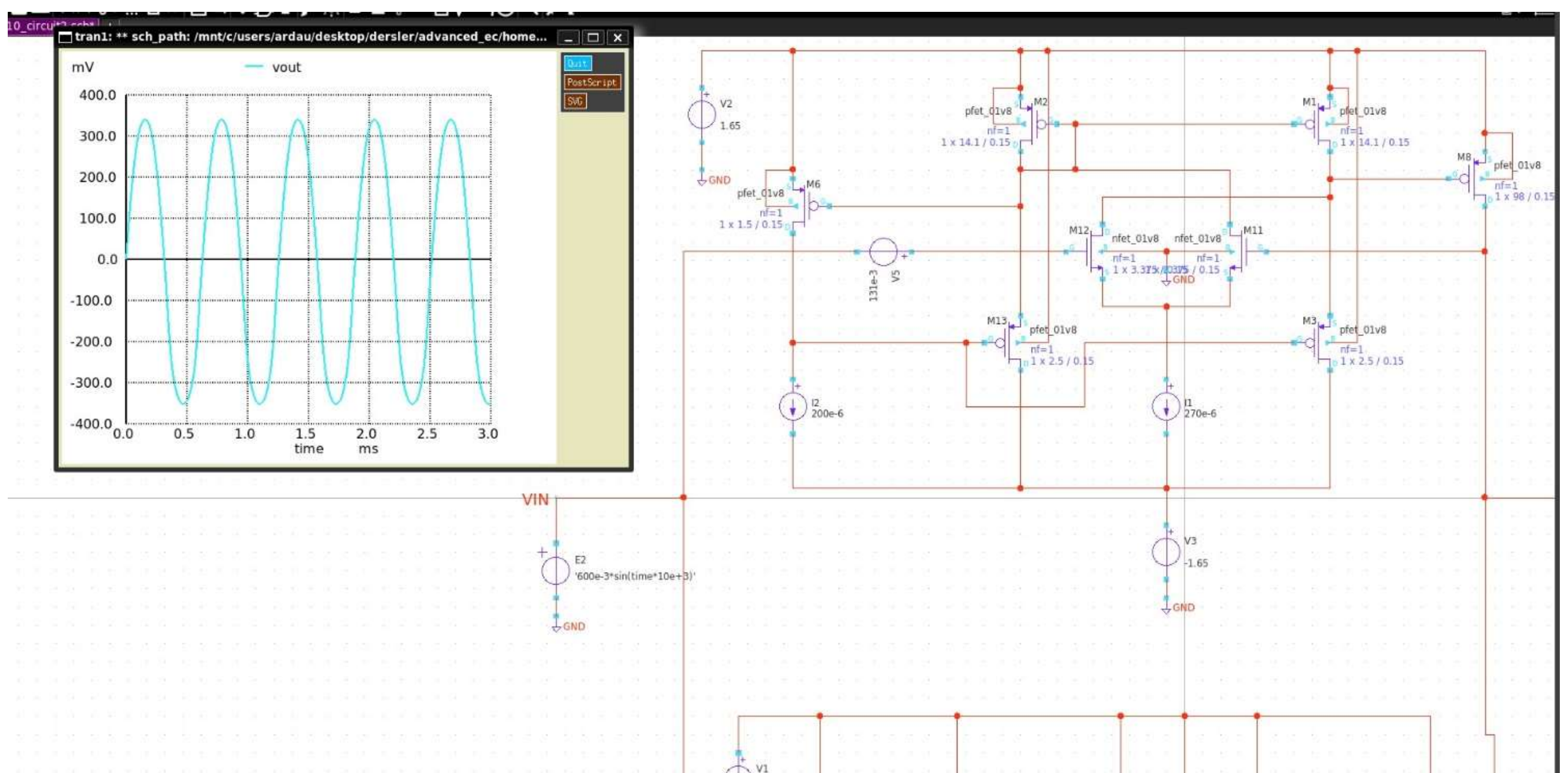




$$f_{v_{in}} = 100 \text{ kHz}$$

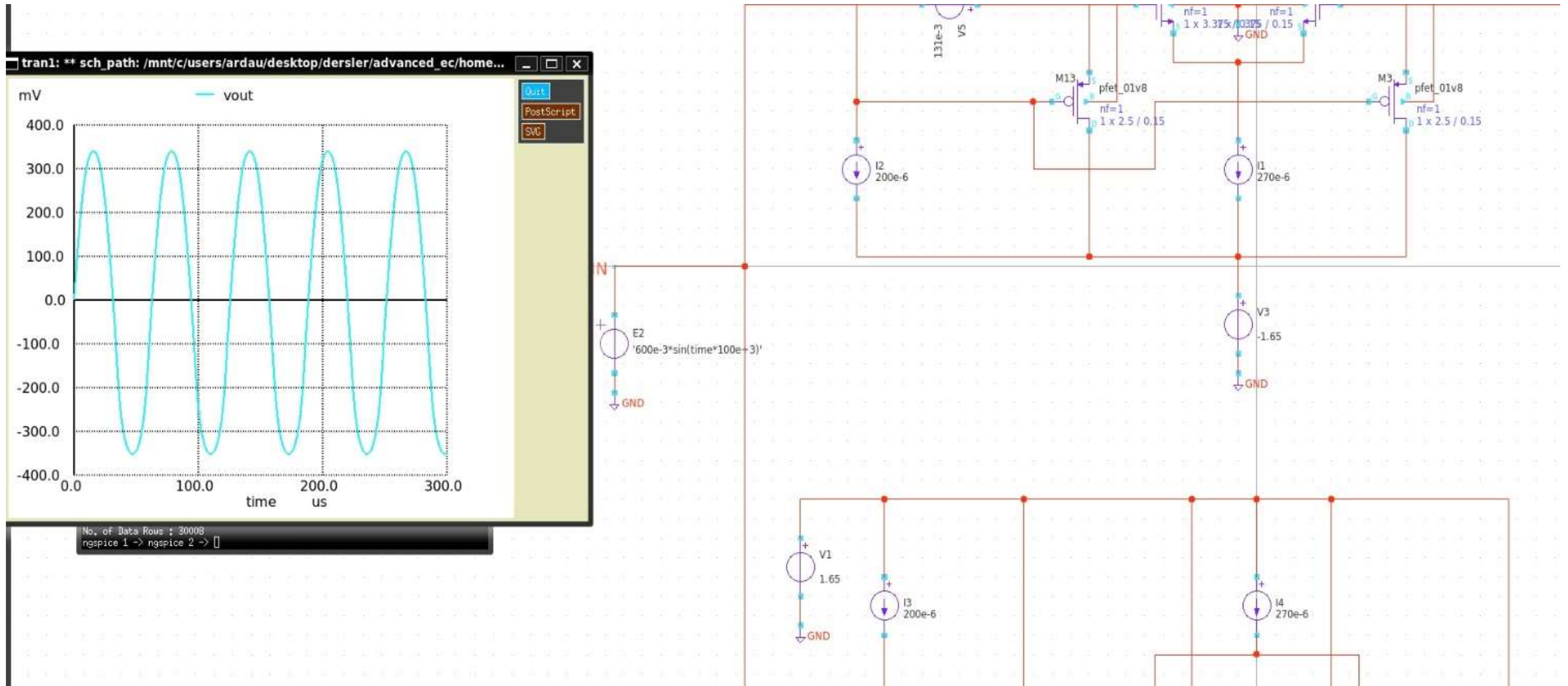


$$f_{v_{in}} = 1 \text{ MHz}$$

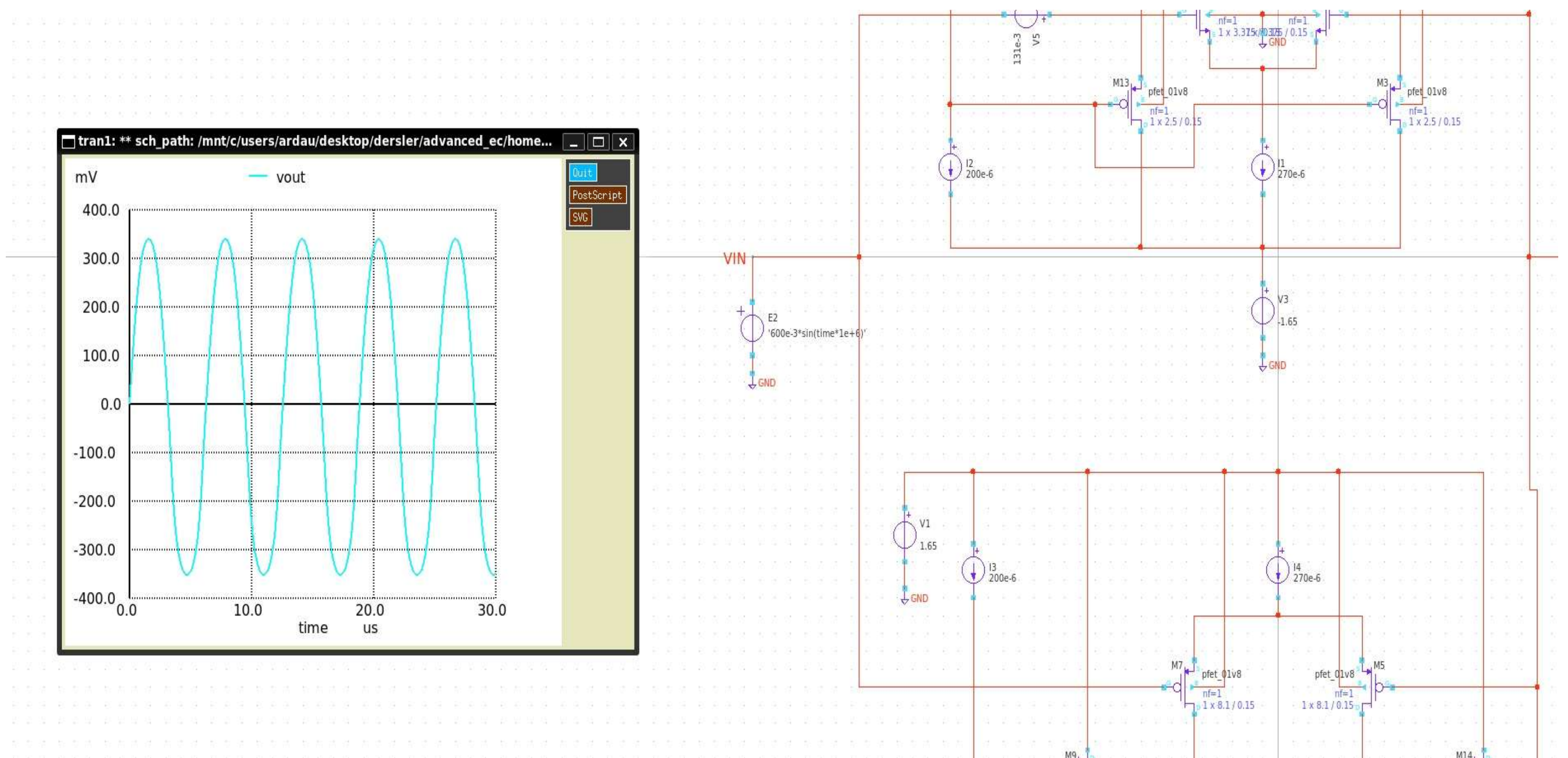




$$f_{vin} = 10 \text{ MHz}$$

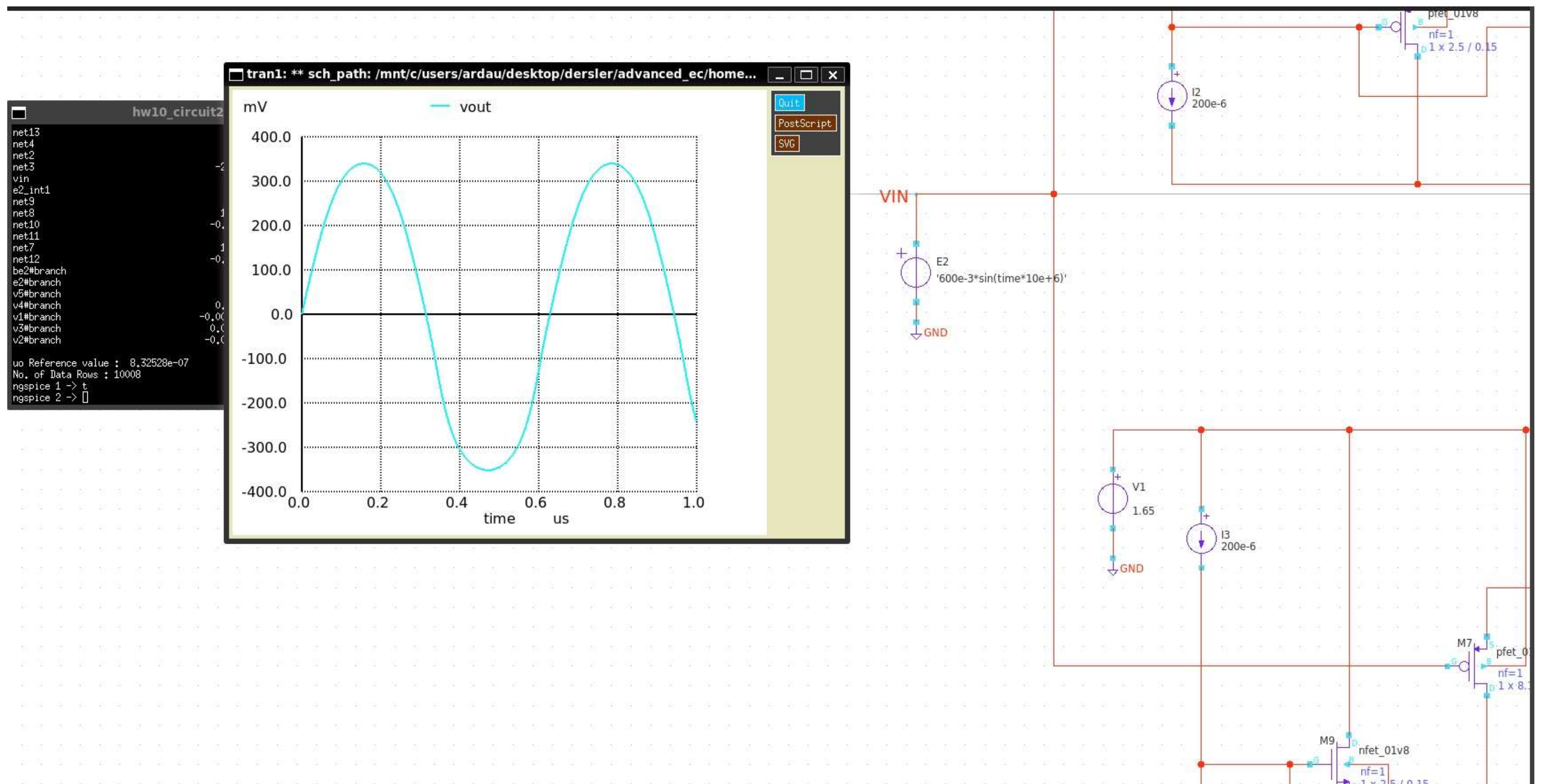


$$f_{vin} = 100 \text{ MHz}$$

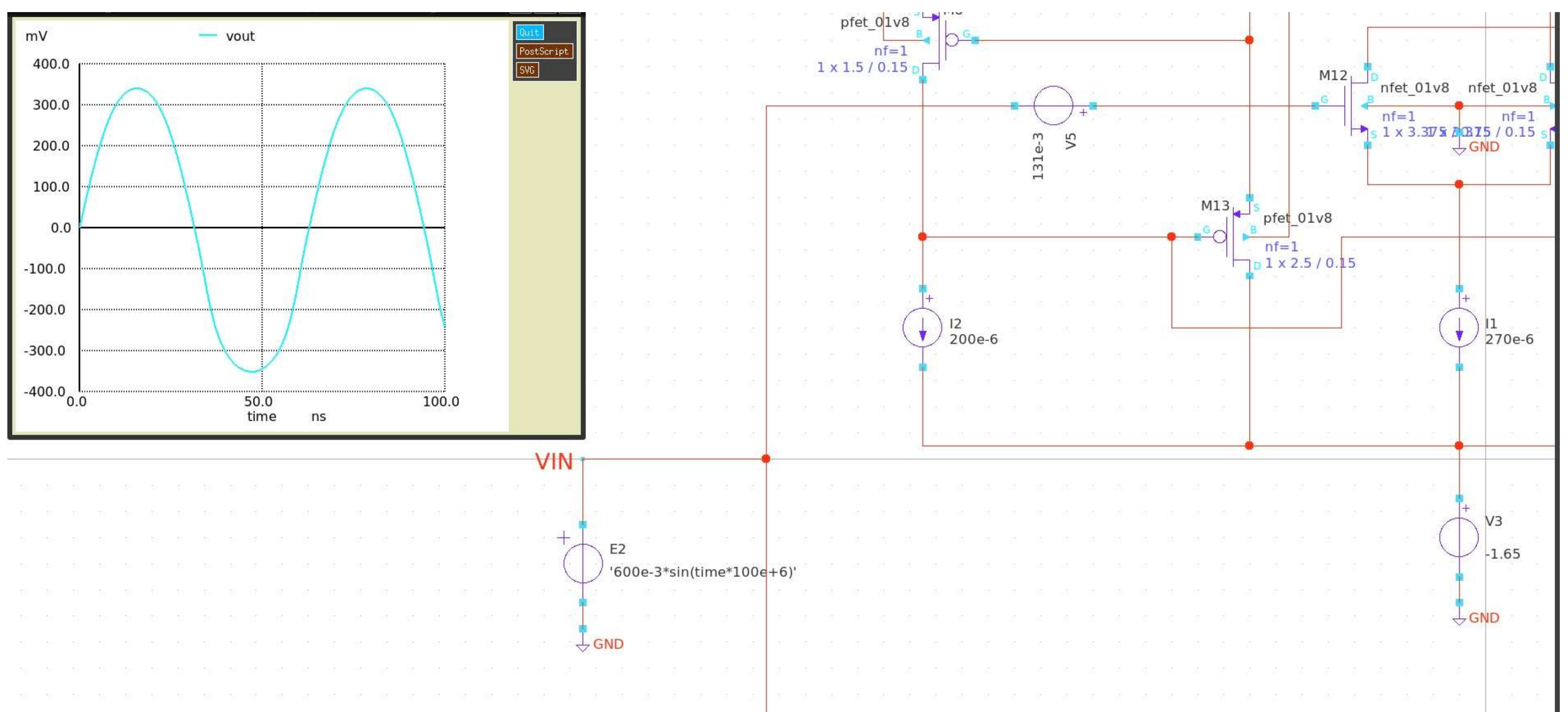




$$f_{V_{in}} = 1 \text{ GHz}$$

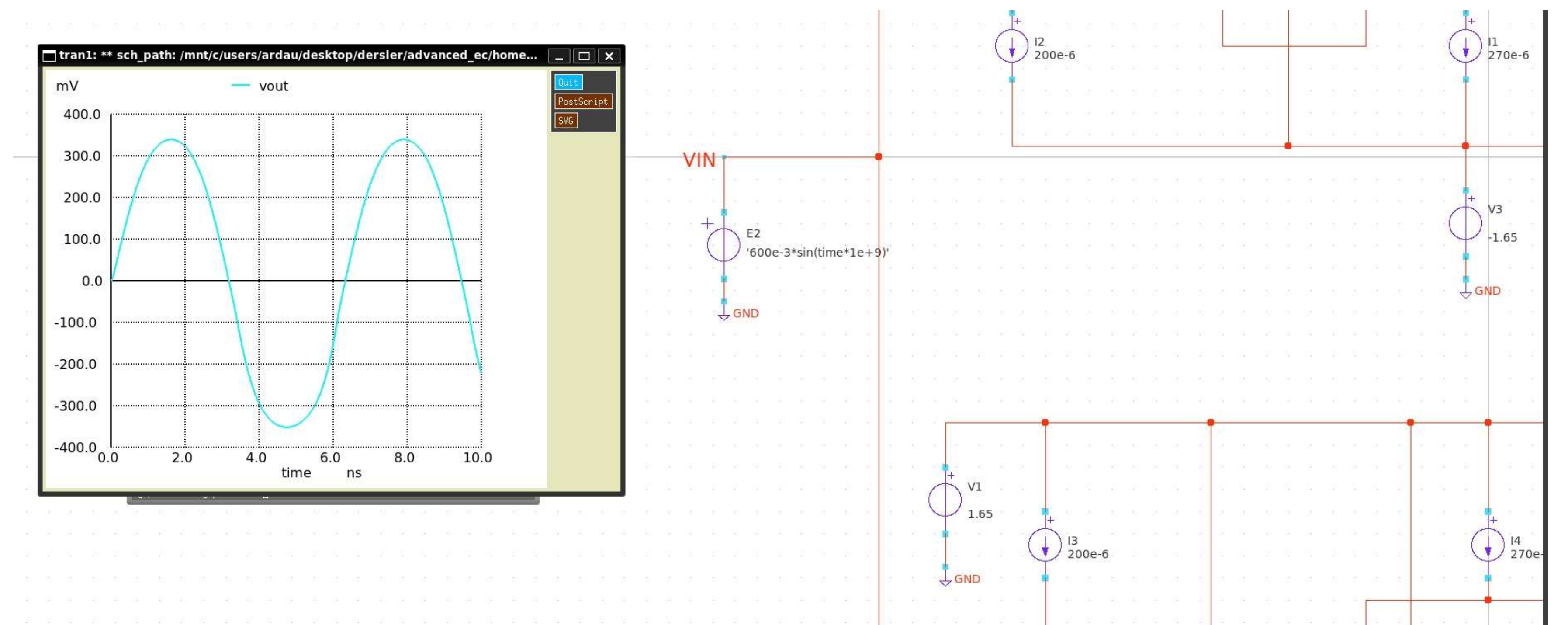


$$f_{V_{in}} = 5 \text{ GHz}$$

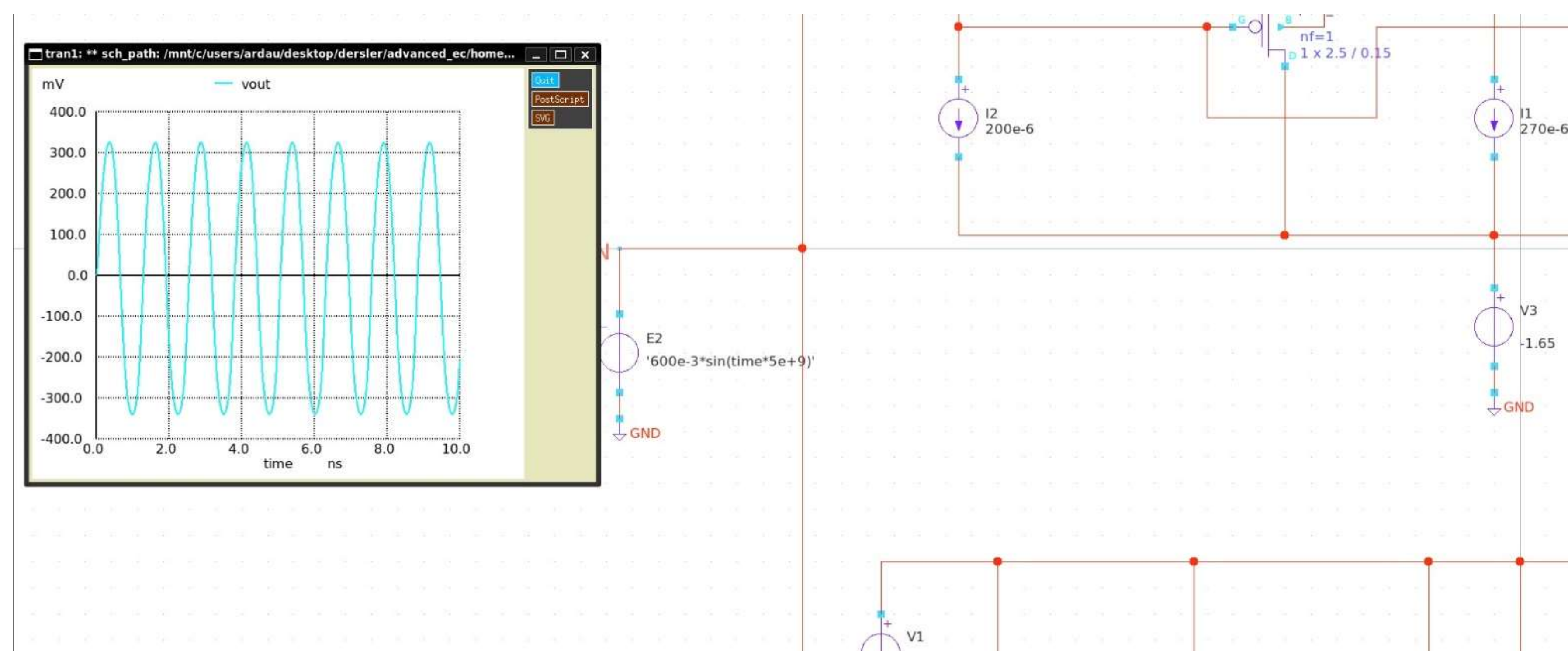



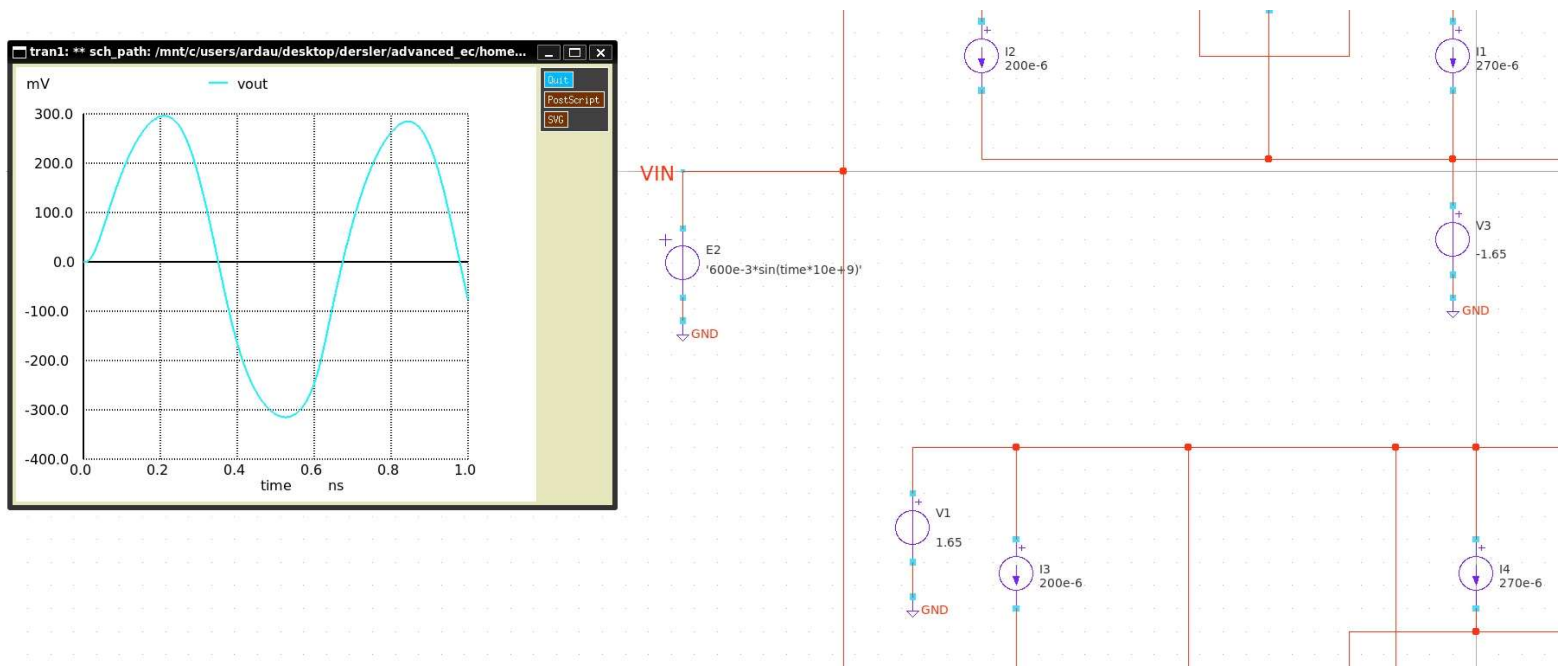$f_{vin} = 10 \text{ GHz} \rightarrow \text{Distortion starts}$



$$P_{in} = 2 \times 200 \times 10^{-6} \times 3.3 = 1.32 \text{ mW}$$

$$P_{out} = \frac{V_{RMS}^2}{R} = \frac{(350 \times 10^{-3} / \sqrt{2})^2}{100} = 0.6125 \text{ mW}$$

$$\Rightarrow \eta = \frac{P_{out}}{P_{in}} \times 100\% = 46.4\% \rightarrow \text{up to } 5 \text{ GHz}$$

For  $f = 5 \text{ GHz}$

$$\eta = 37.585\%$$

For  $f = 10 \text{ GHz}$

$$\eta = 34.1\%$$