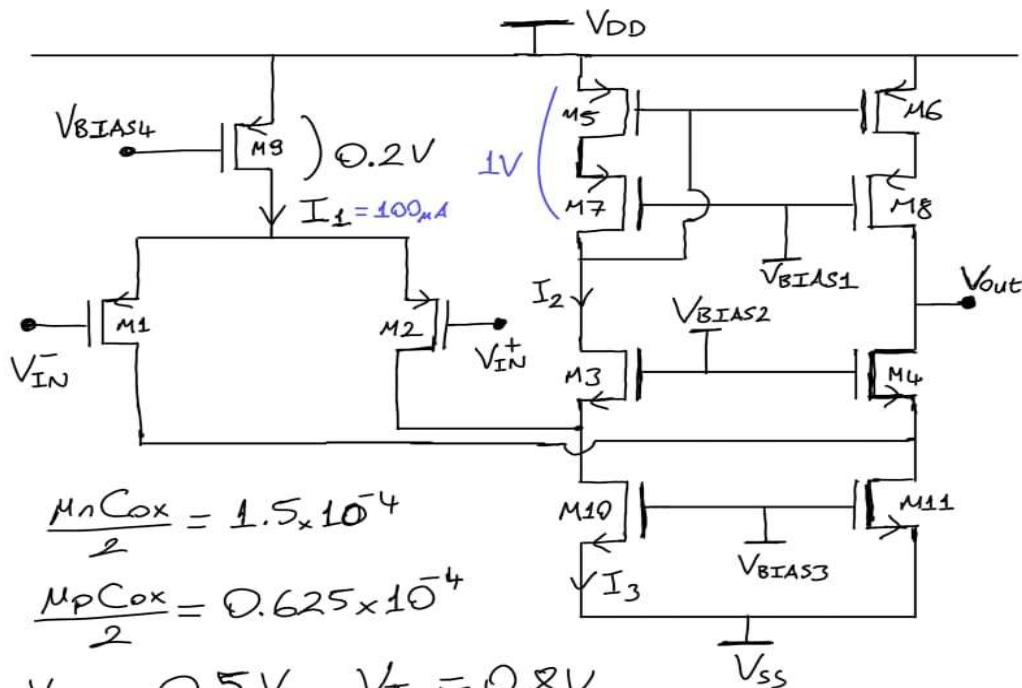


HOMework 9

ARDA ÜNAL



→ Bias current through M9 is $100\mu A$, so

$$\left(\frac{W}{L}\right)_9 = 40 \text{ assuming } V_{ov}^{\min} = 0.2V$$

$$\Rightarrow V_{BIAS4}^{\min} = V_{DD} - 1V$$

→ Since M1 and M2 will carry $50\mu A$, then

$$\left(\frac{W}{L}\right)_{1,2} = 20, \text{ again assuming } V_{ov}^{\min} = 0.2V$$

$$\Rightarrow V_{BIAS+,-} = V_{DD} - 0.2V - 1V = V_{DD} - 1.2V$$

→ $V_{ov10-11} = 0.5V$ and they will carry $100\mu A$ each, thus

$$\left(\frac{W}{L}\right)_{10-11} = 2.667 \text{ and } V_{BIAS3} = 0.5 + 0.5 + V_{SS} = 1V + V_{SS}$$

→ For M3 and M4, $V_{ov} = 0.2 V$, so

$$V_{source,3,4}^{min} = 0.5 V, \quad V_{source,3,4}^{max} = V_{DD} - 0.4 V$$

→ Thus to be in pinch-off region

$$V_{BIAS2} = 0.5 + 0.7 = 1.2 V$$

$$\left(\frac{W}{L}\right)_{3,4} = 8.334$$

→ For M5 to be in pinch-off region,

$$V_{DS}^{M5} + V_{DS}^{M7} \geq 1 V, \quad \text{thus if we assume that}$$

$$V_{ov}^{M5} = 0.2 V, \quad \text{then} \quad V_{ov}^{M7} = 0.8 V$$

$$\Rightarrow \left(\frac{W}{L}\right)_{5,6}^{max} = 20 \quad \text{and} \quad \left(\frac{W}{L}\right)_{7,8}^{min} = 1.25$$

$$\text{and } V_{BIAS1}^{min} = V_{DD} - 1 V$$

→ To extend working range of circuit, we can choose middle of the operating range for bias voltages:

$$V_{out}^{max} = V_{DD} - 1, \quad V_{out}^{min} = V_{SS} + 0.7 V$$

→ Let $V_{DD} = 3.3 V$ and $V_{SS} = 0 V$, then

$$V_{out}^{max} = 2.3 V \quad \text{and} \quad V_{out}^{min} = 0.7 V$$


$$\rightarrow V_{BIAS+,-} = \frac{V_{DD} - 0.2 - 0.5}{2} = 1.3 V$$

$$\rightarrow V_{BIAS1} = 1.65 V \quad \text{and} \quad V_{BIAS2} = 1.2 V$$

$$GBW = \frac{g_{m1}}{2\pi C_L} \Rightarrow g_{m1} = 7.746 \times 10^{-4} S$$

$$\Rightarrow GBW = 61.6 MHz$$

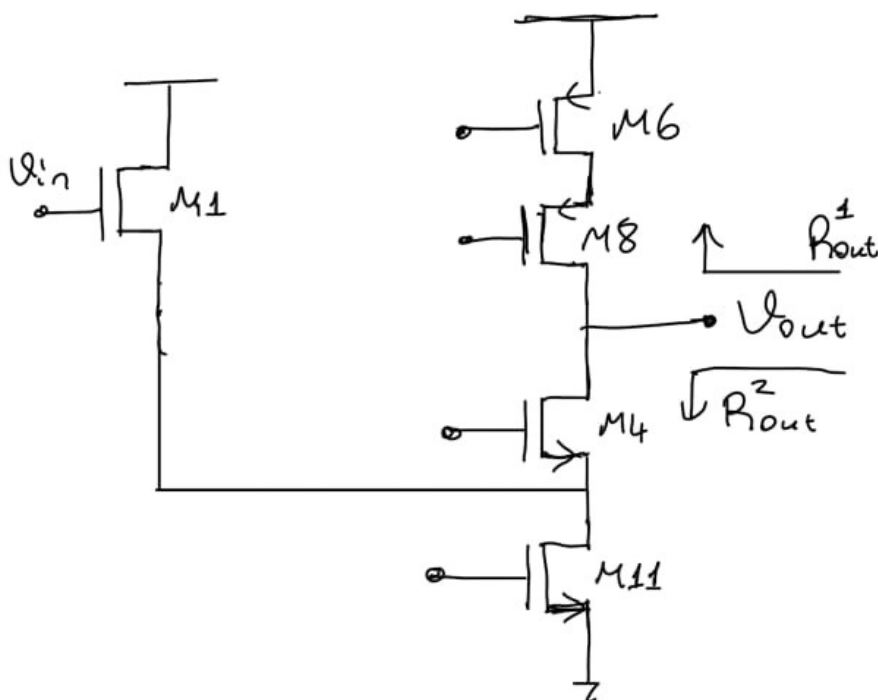→ To calculate the gain, we should find R_{out} .



$$\Rightarrow R_{out} = R_{out}^1 \parallel R_{out}^2$$

$$\Rightarrow R_{out}^1 = g_{m8} r_{o8} r_{o6}, \quad R_{out}^2 = g_{m4} r_{o4} (r_{o11} \parallel r_{o1})$$

$$\Rightarrow A_v = -g_{m1} [g_{m8} r_{o8} r_{o6} \parallel g_{m4} r_{o4} (r_{o11} \parallel r_{o1})]$$

$$r_o = \frac{V_A}{I_D} = \frac{V_{EL}}{I_D} \quad \text{and} \quad g_m = \sqrt{2k' \frac{W}{L} I_D}$$

→ V_E values for NMOS and PMOS for V_{GS} 's are

$$\rightarrow V_{GS}^P = 1.6 \Rightarrow V_E^P = 29700260$$

$$\rightarrow V_{GS}^P = 1.8 \Rightarrow V_E^P = 31642515$$

$$\rightarrow V_{GS}^N = 1 \Rightarrow V_E^N = 83029850$$

$$\rightarrow V_{GS}^N = 0.7 \Rightarrow V_E^N = 36505350$$

$$\Rightarrow r_{o11} = 124.5 k\Omega, \quad r_{o1} = 316.4 k\Omega$$

$$\Rightarrow r_{o4} = 109.5 k\Omega, \quad r_{o8,6} = 297 k\Omega$$

$$\Rightarrow g_{m4} = 5 \times 10^{-4} \text{ S}, \quad g_{m5} = 1.25 \times 10^{-4} \text{ S}$$

$$\text{and } g_{m1} = 5 \times 10^{-4} \text{ S}$$

$$\Rightarrow R_{out}^1 = 11 \text{ M}\Omega, \quad r_{o11} // r_{o1} = 89.3 \text{ k}\Omega$$

$$\Rightarrow R_{out}^2 = 4.89 \text{ M}\Omega$$

$$\Rightarrow A_v = -1692.5$$

→ Bandwidth can be calculated via

$$BW = \frac{GBW}{A_v} = \frac{61.6 \text{ MHz}}{1692.5} \cong 36.4 \text{ kHz}$$

→ I have changed the bias voltages to find an appropriate DC operating point and I played with the $(\frac{W}{L})$ value of $M_{10,11}$ for the same reason. I increased $(\frac{W}{L})$ ratio of $M_{1,2}$ to increase g_m means that I increased GBW.

→ According to simulation results,

$$A_v = 59.1 \text{ dB} = 901.5$$

$$GBW = 54 \text{ MHz}$$


$$BW \cong 54 \text{ kHz } (-3\text{dB})$$

FOM for hand calculation:

$$FOM = \frac{GBW \times C_L}{I_{BIAS}} = 1232$$



→ For simulation: $FOM = 1040$

→ For layout post-sim: $FOM =$

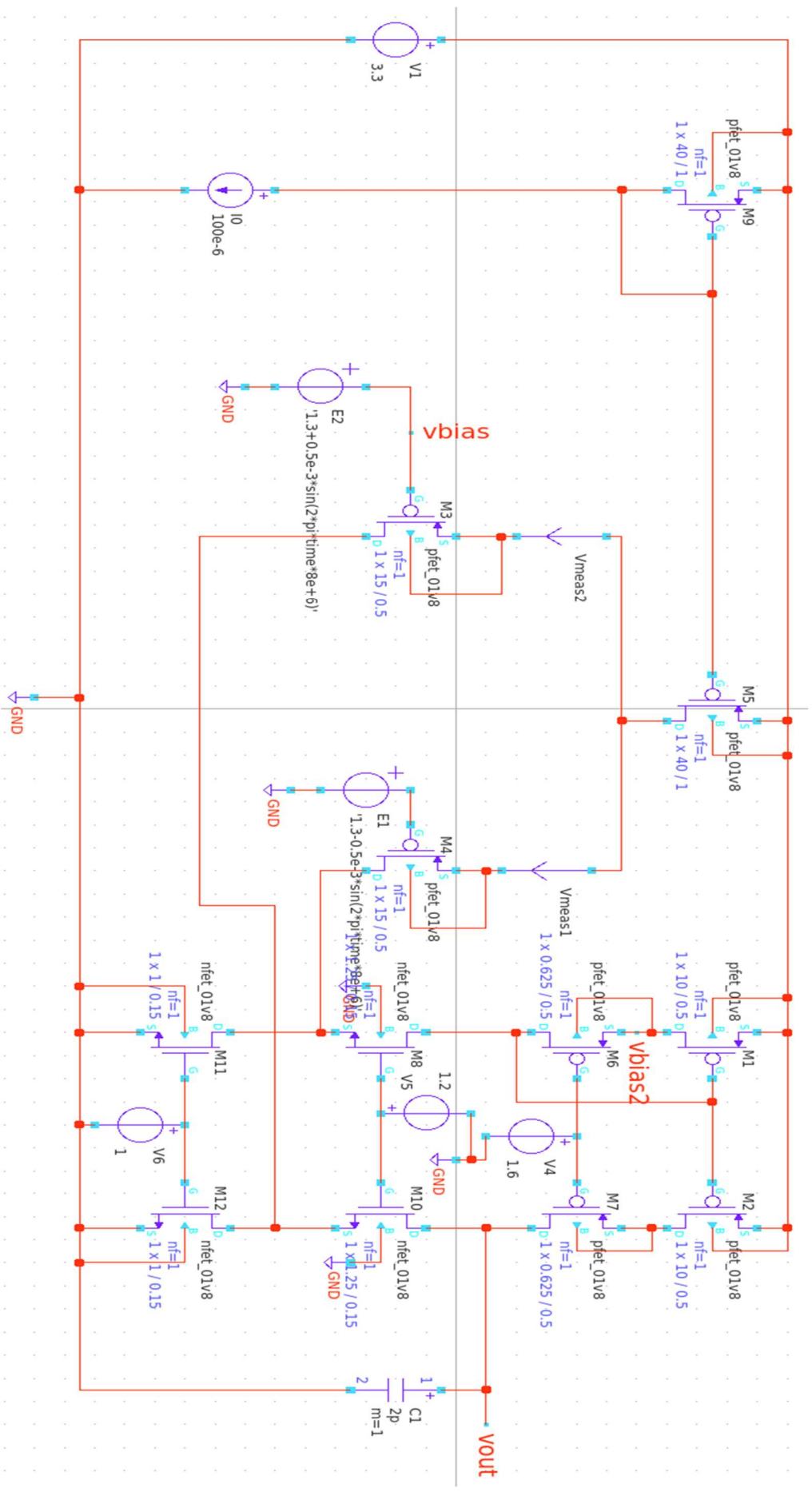

y9_db.sch+ untitled.sch+ +
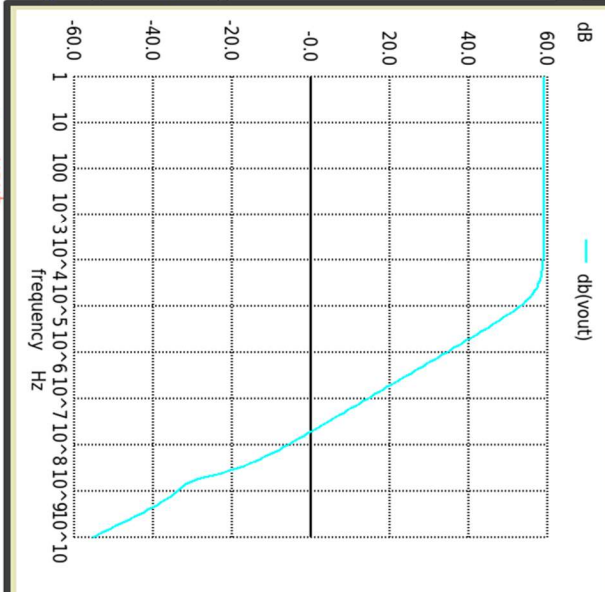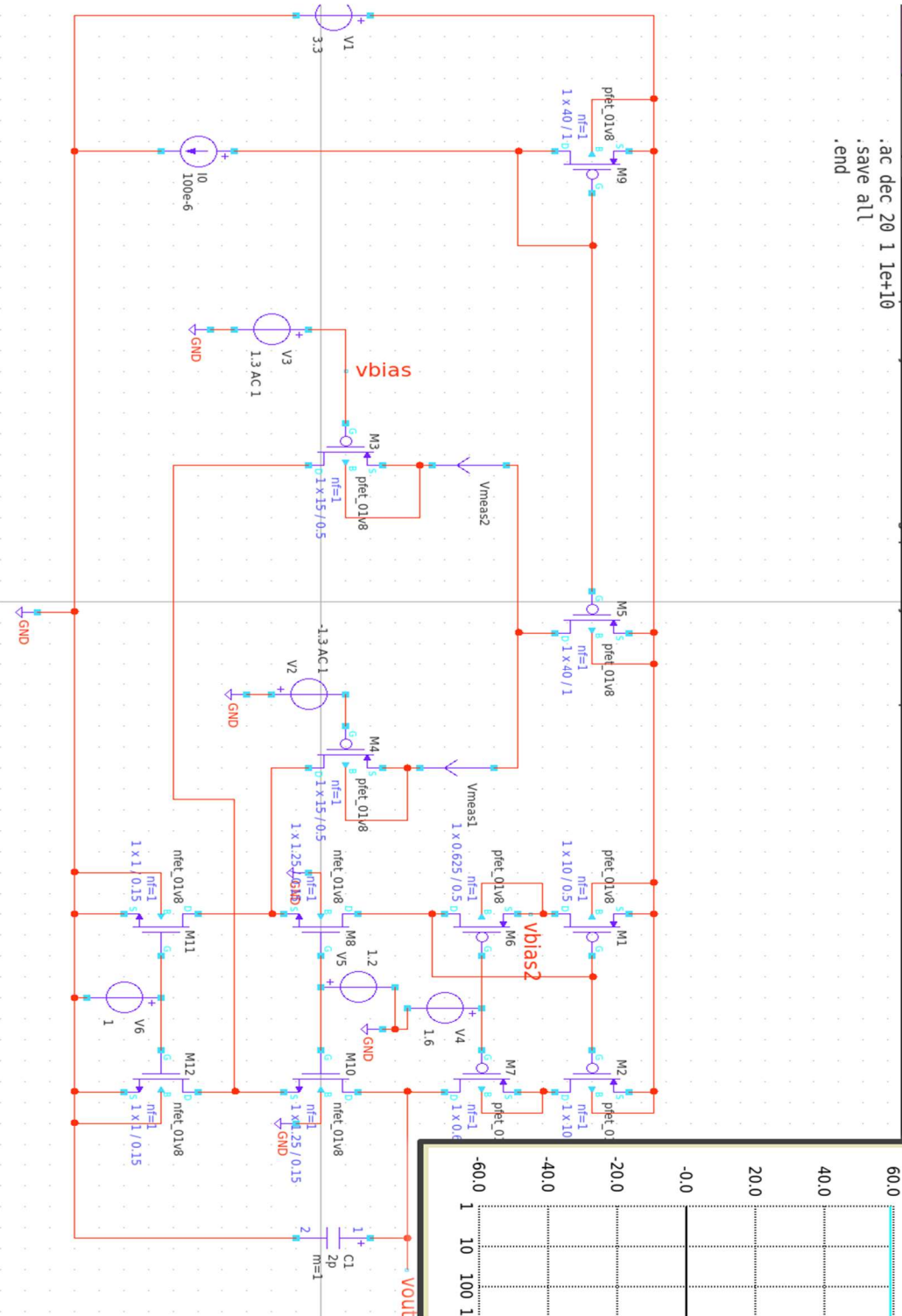
```
.ac dec 20 1 1e+10
.save all
.end
```





hw9_db.spice+ -a || sh - [X]
Note: Dynamic gain stepping completed
Reference value : 1.00000e+00
No. of data rows : 201
respsice 1 -> plot db(vout)
respsice 2 -> plot db(vout)
x0 = 4.56155e+07, g0 = 0
x0 = 5.21855e+07, g0 = 0

```

.model /model/cd/udm/puk/sky130M/level1/magp130/sky130
.tran 1u 10m
.save all
.end


```

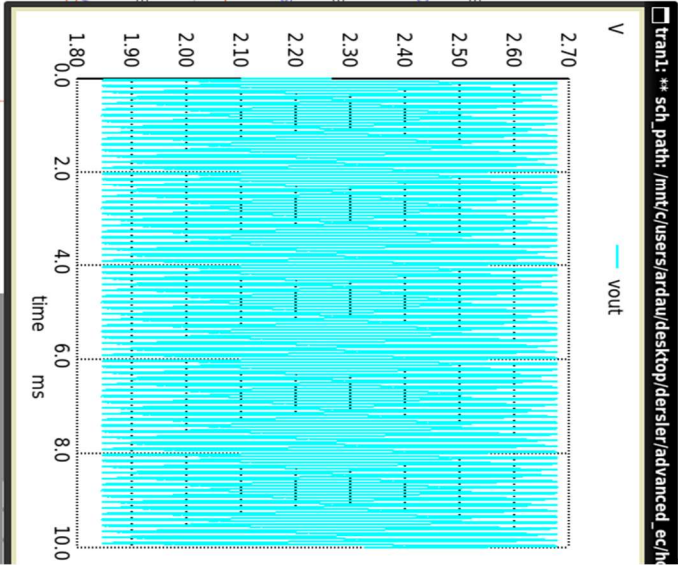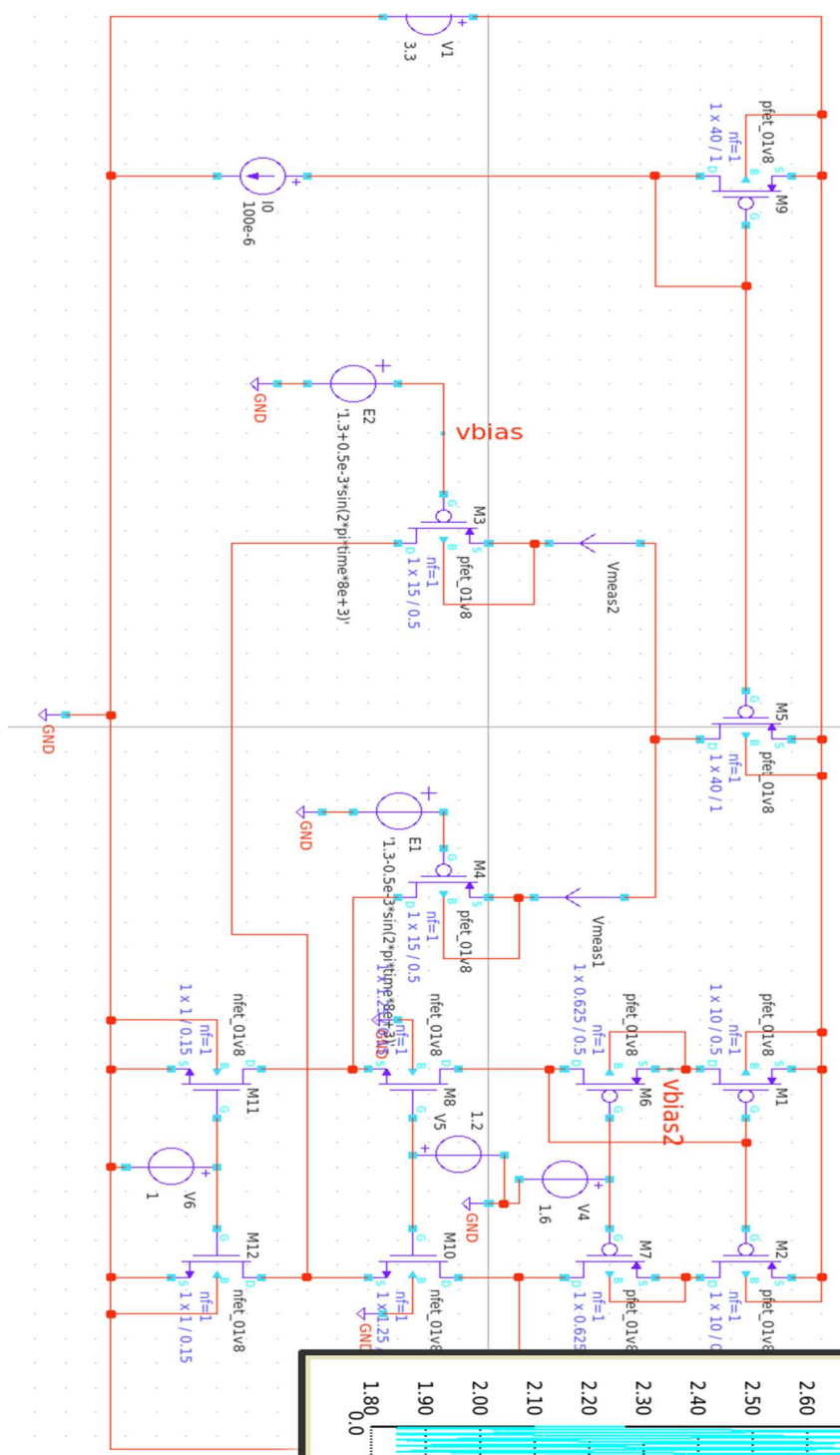


```

vmeas1:branch
v1:branch
Reference value : 5.65522e-03
No. of data rows : 10008
respic1 1 -> Plot vout
respic2 2 ->

```

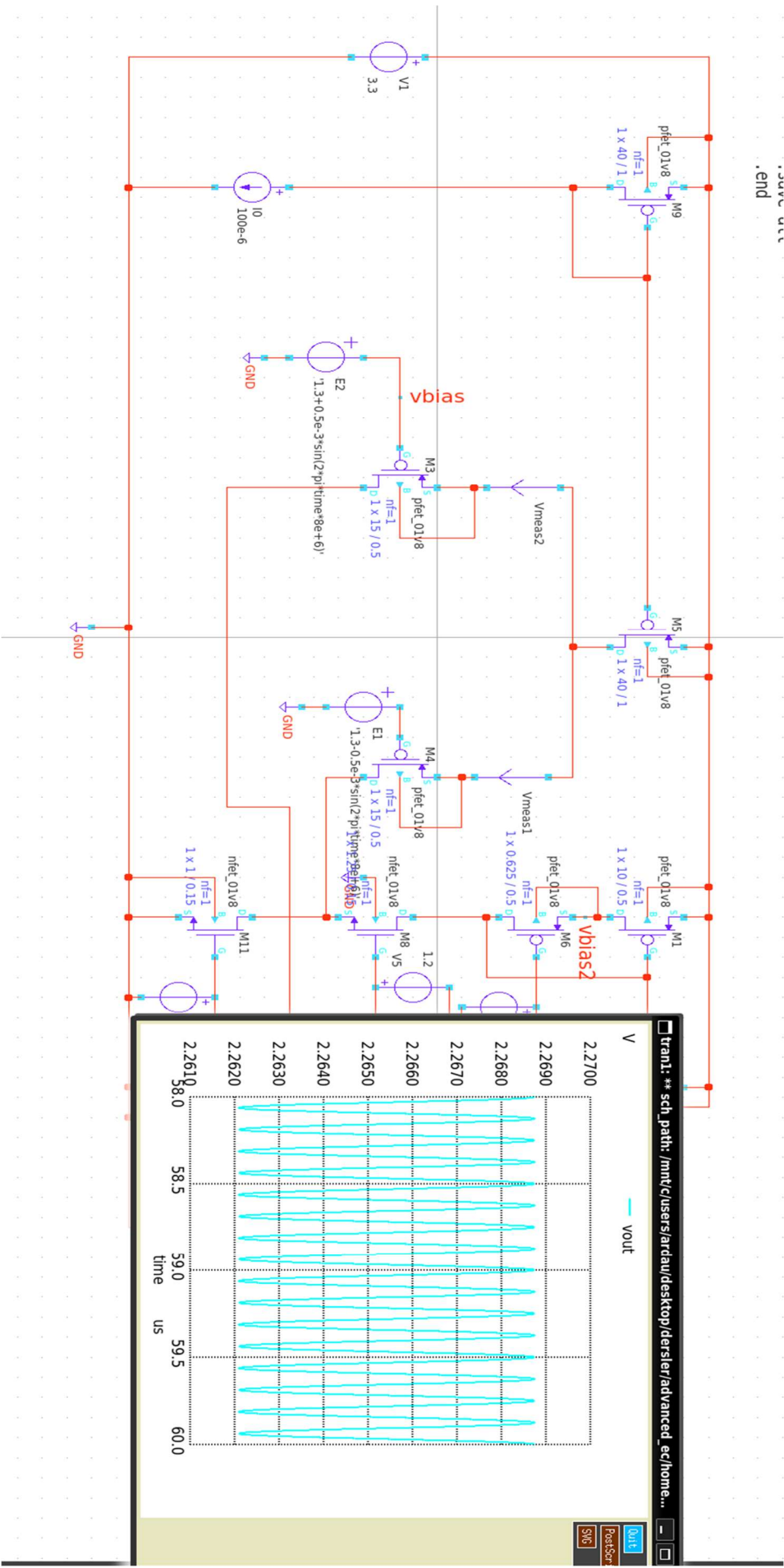
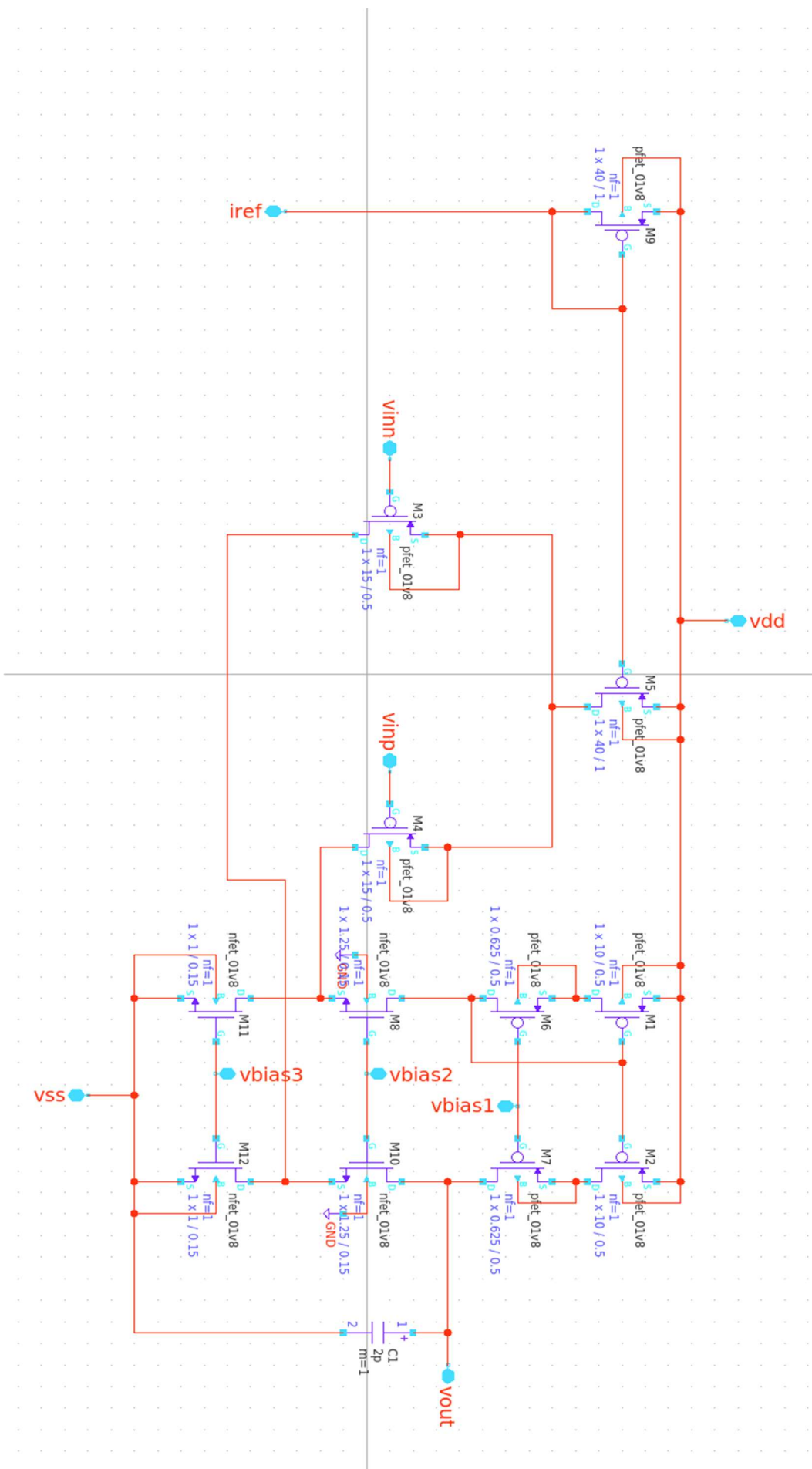
```
.lib /home/ardau/pdk/sky130A/libs.tech/ngspice/sky130.lib.spice tt
.ac dec 20 1 1e+10
.save all
.end
```

