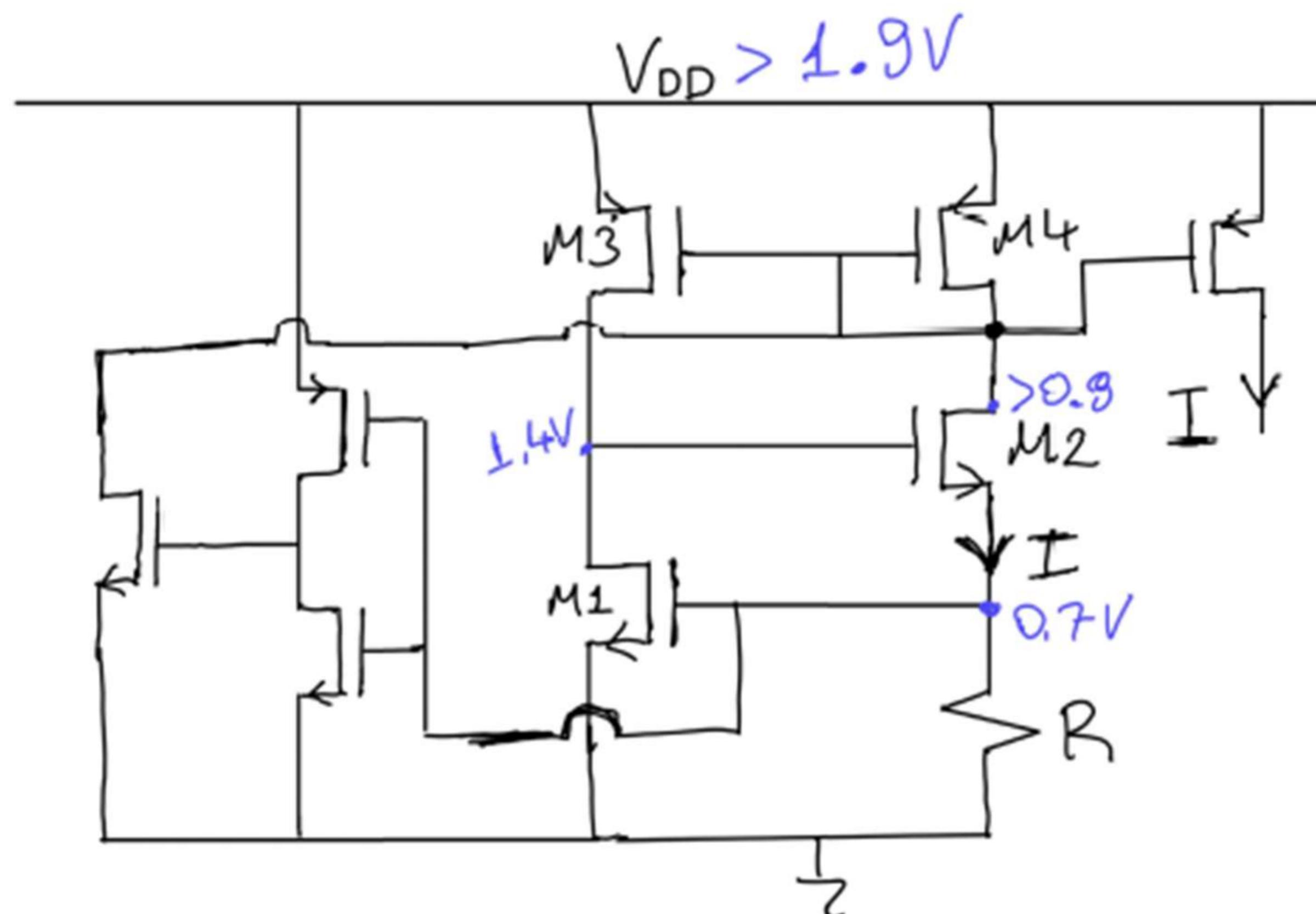


HOMEWORK 7

ARDA ÜNAL

7.1 >



$$V_{GS1} = RI \quad V_{TN} = 0.5V \text{ and } V_{TP} = 0.8V$$

$$\Rightarrow V_{GS1} = 0.7V \text{ and } I = 10^{-4}A \Rightarrow R = 7k\Omega$$


$$V_{GS1} = V_{TN} + \sqrt{\frac{2IL_1}{\mu_n C_o \times W_1}} \Rightarrow \left(\frac{W}{L}\right)_1 = 16.667$$

Let all $V_{ov} = 0.2$, then

$$\left(\frac{w}{L}\right)_3 = \left(\frac{w}{L}\right)_4 = 4.167, \quad \left(\frac{w}{L}\right)_2 = \left(\frac{w}{L}\right)_1$$

→ To achieve an acceptable result, I played with

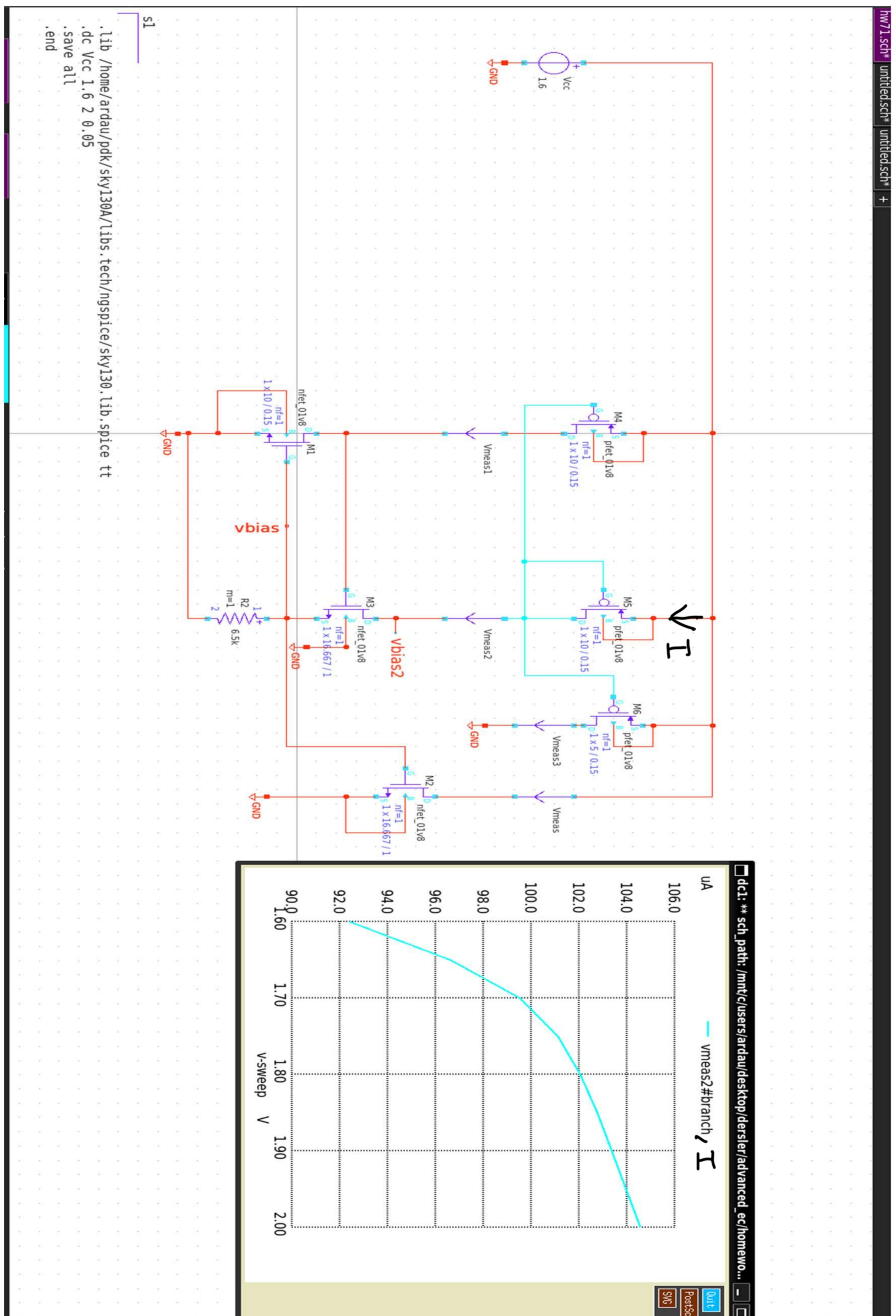$\left(\frac{w}{L}\right)_1$, $\left(\frac{w}{L}\right)_{3 \text{ and } 4}$ and R.




```


.s1
.lib /home/ardau/pdk/sky130A/libs.tech/ngspice/sky130.lib spice tt
.dc Vcc 1.6 2 0.05
.save all
.end


```

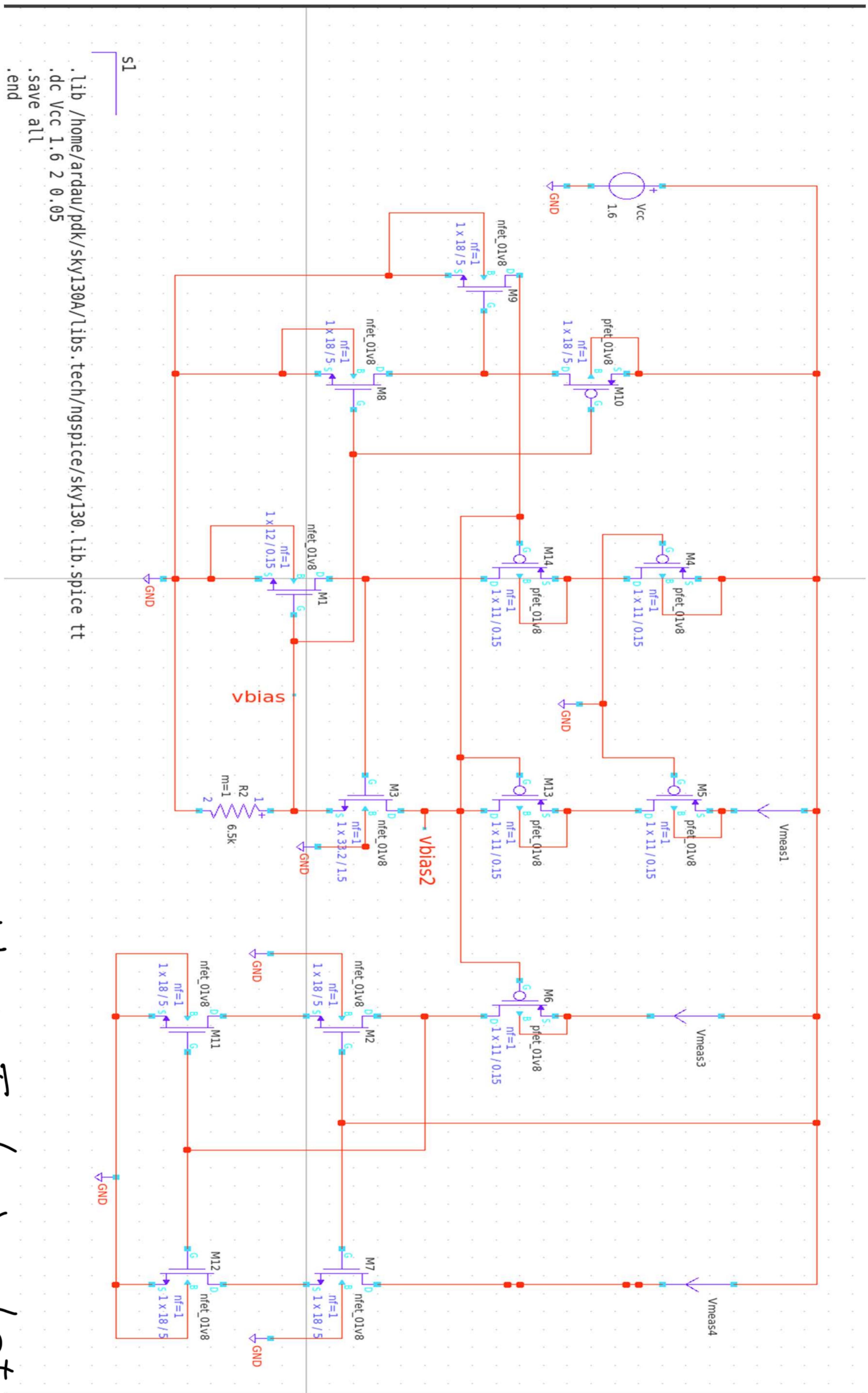
Cascaded current mirrors combined with startup circuit



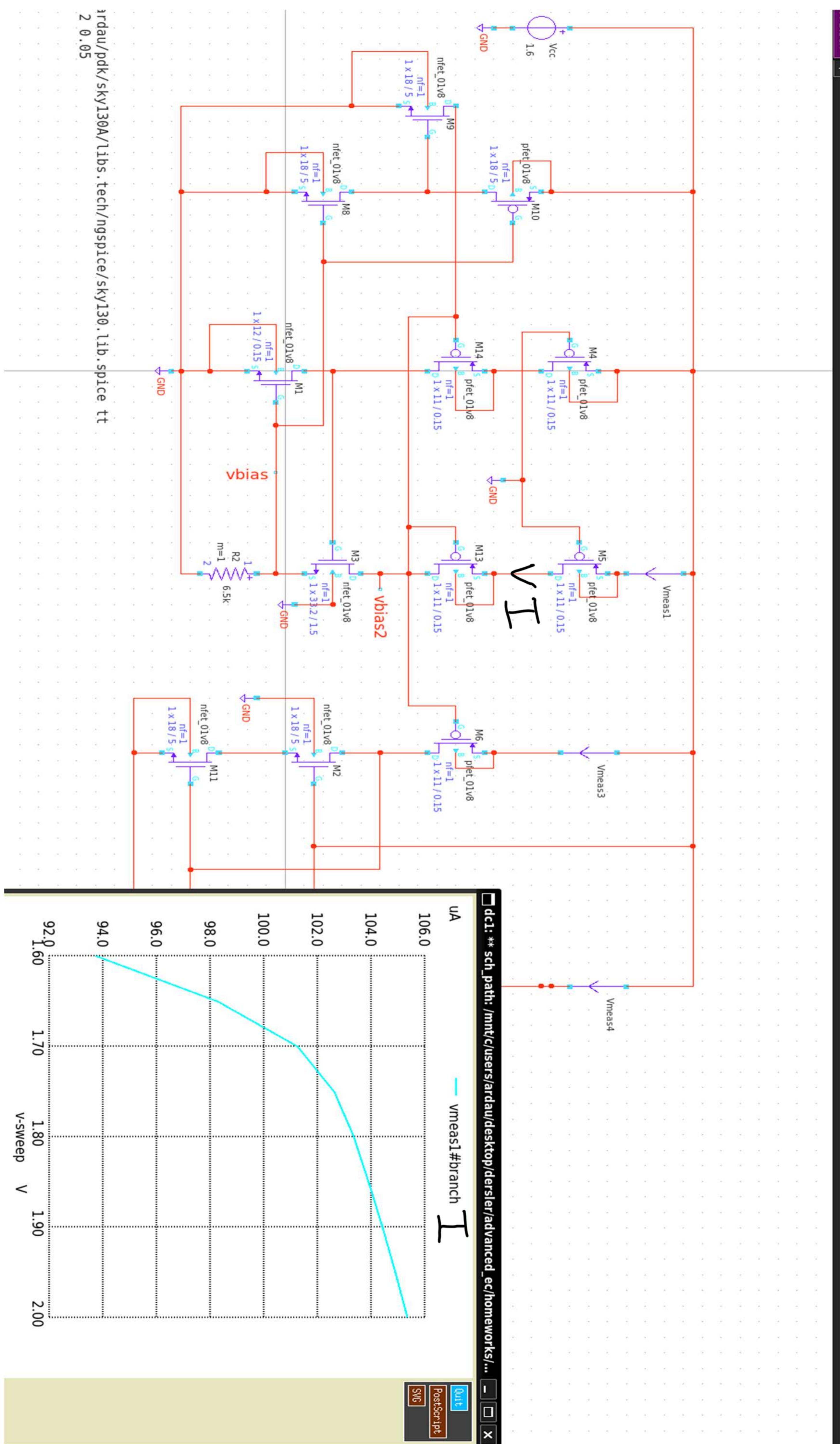I have used NMOS current mirrors that I designed at HW where the reference current was 100mA.



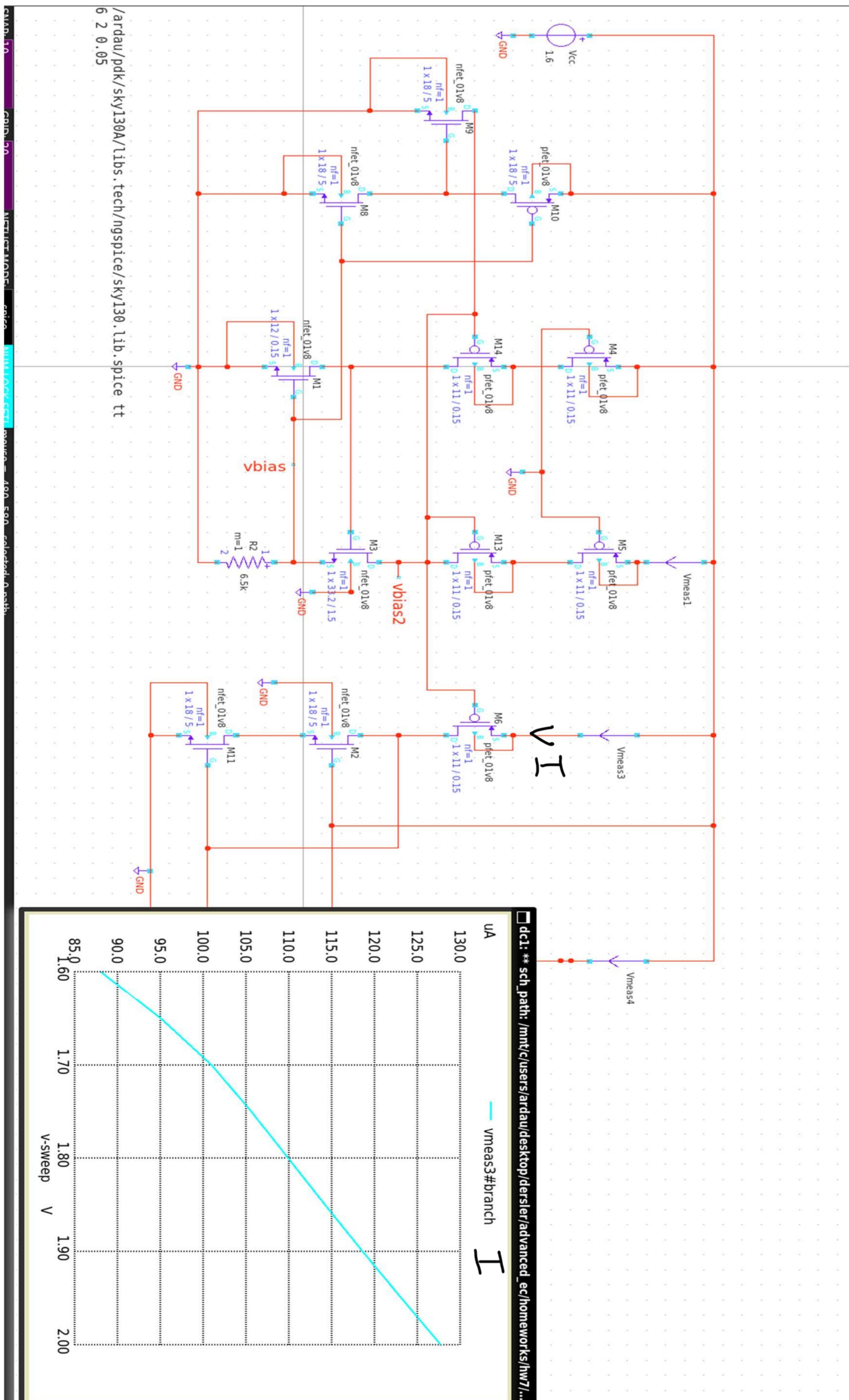


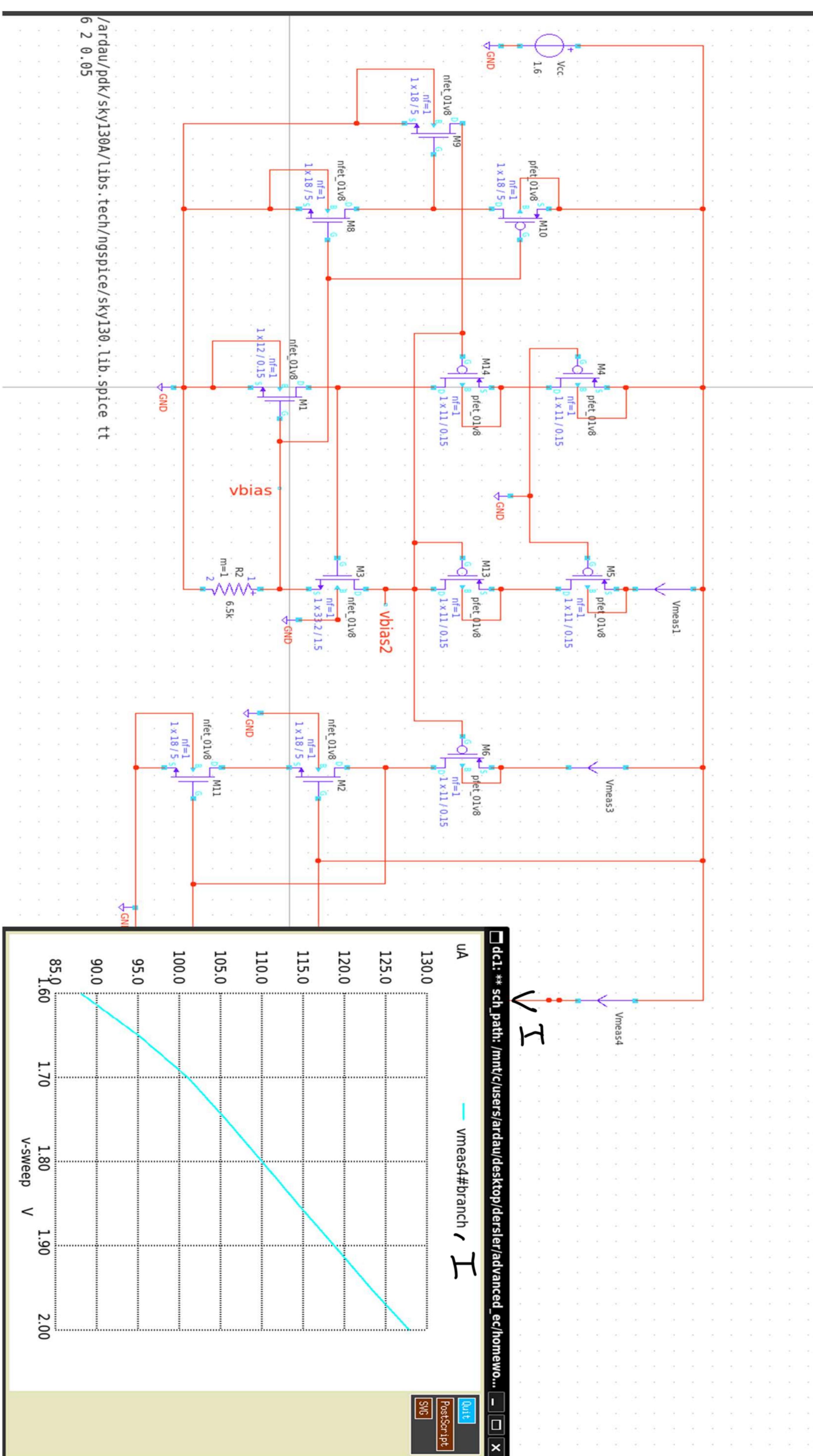

2)

V_{CC}

→ I designed Brokaw
Bandgap reference.

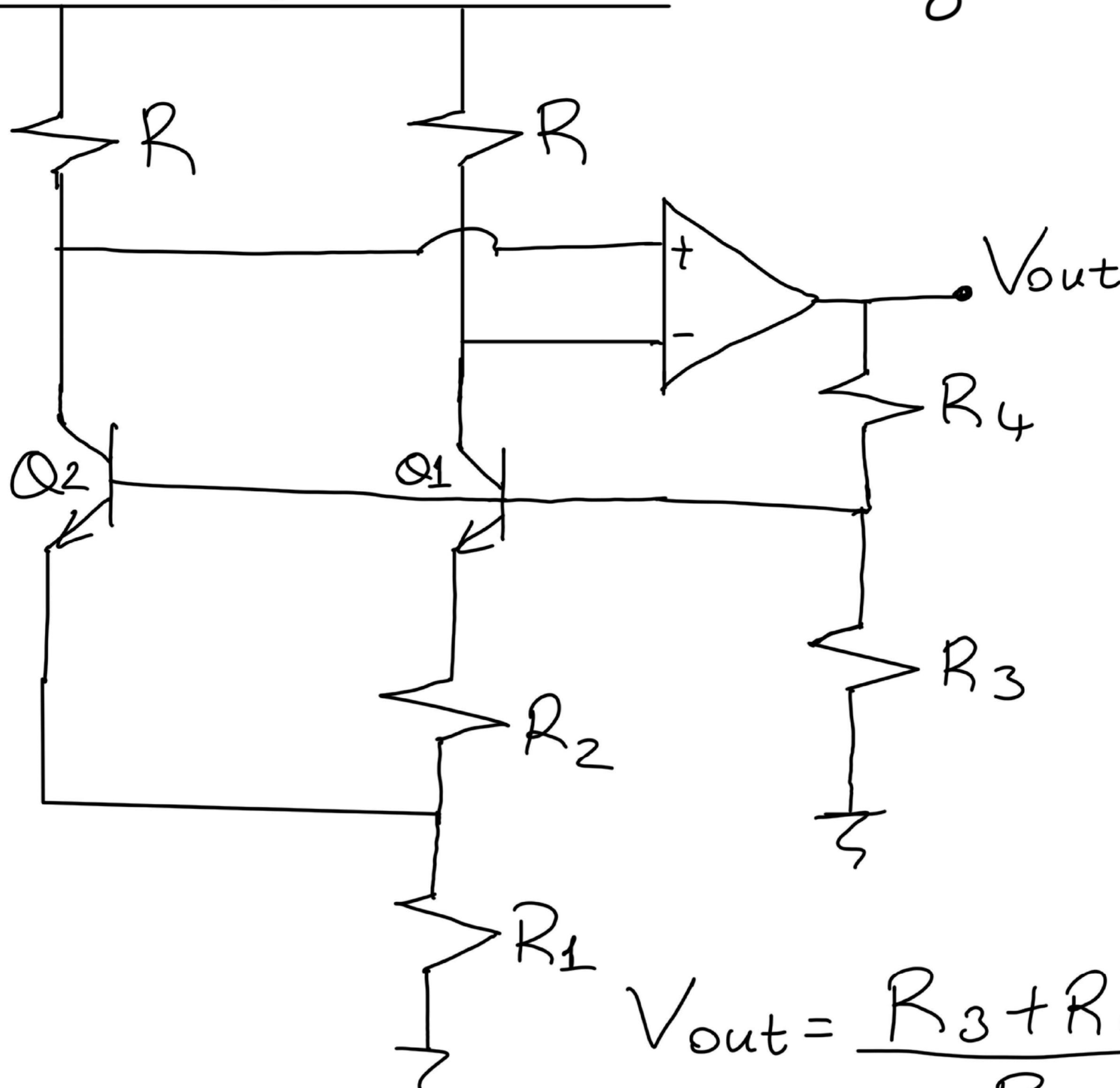

$$V_{out} = \frac{R_3 + R_4}{R_3} V_{ref}$$

$$V_{ref} = V_{BE} + V_{R1} = V_{BE} + 2 \frac{R_1}{R_2} V_{R2}$$

$$\Rightarrow V_{ref} = \underbrace{V_{BE}}_{CTAT} + 2 \frac{R_1}{R_2} \underbrace{\frac{kT}{q} \ln 8}_{PTAT}$$

$$\frac{\partial V_{BE}}{\partial T} = -2 \text{mV} \Rightarrow 2 \frac{R_1}{R_2} \frac{k}{q} \ln 8 = 2 \times 10^{-3}$$

$$\Rightarrow \frac{R_1}{R_2} = 5.58 \Rightarrow R_1 = 5.58 k\Omega \quad R_2 = 1 k\Omega$$


$$\Rightarrow V_{ref} \approx 1.2V \Rightarrow \frac{1.3}{1.2} = 1 + \frac{R_4}{R_3} \Rightarrow \frac{R_4}{R_3} = 0.083$$

$$\Rightarrow \frac{R_3}{R_4} = 12 \rightarrow \text{There was a PTAT slope, so}$$


I decreased ratio of R_1/R_2 and V_{ref} was $1.149V$

thus I also play with ratio of $\frac{R_3}{R_4}$ to have $V_{out} = 1.3V$.

Calculated values have PTAT slope

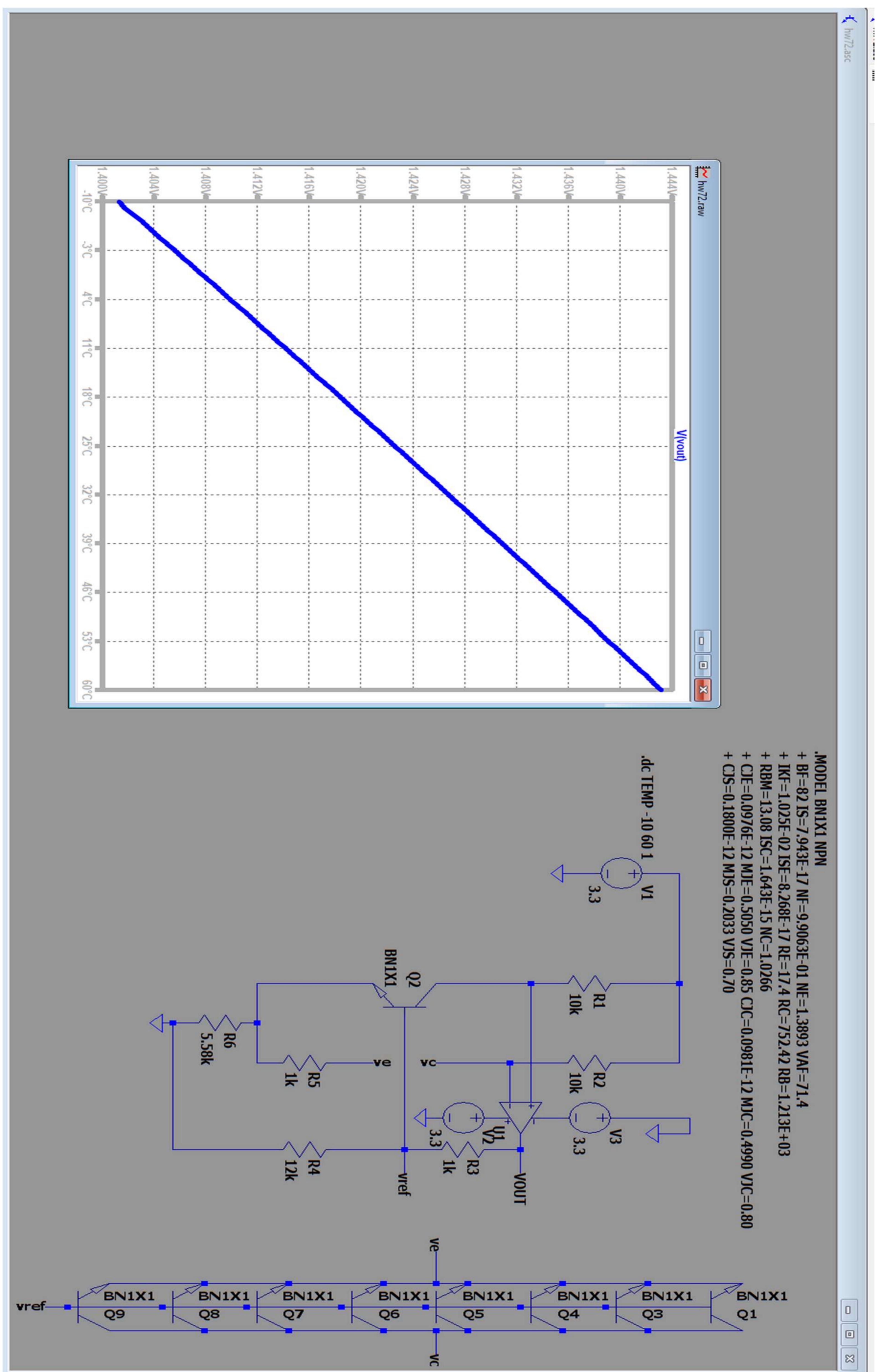

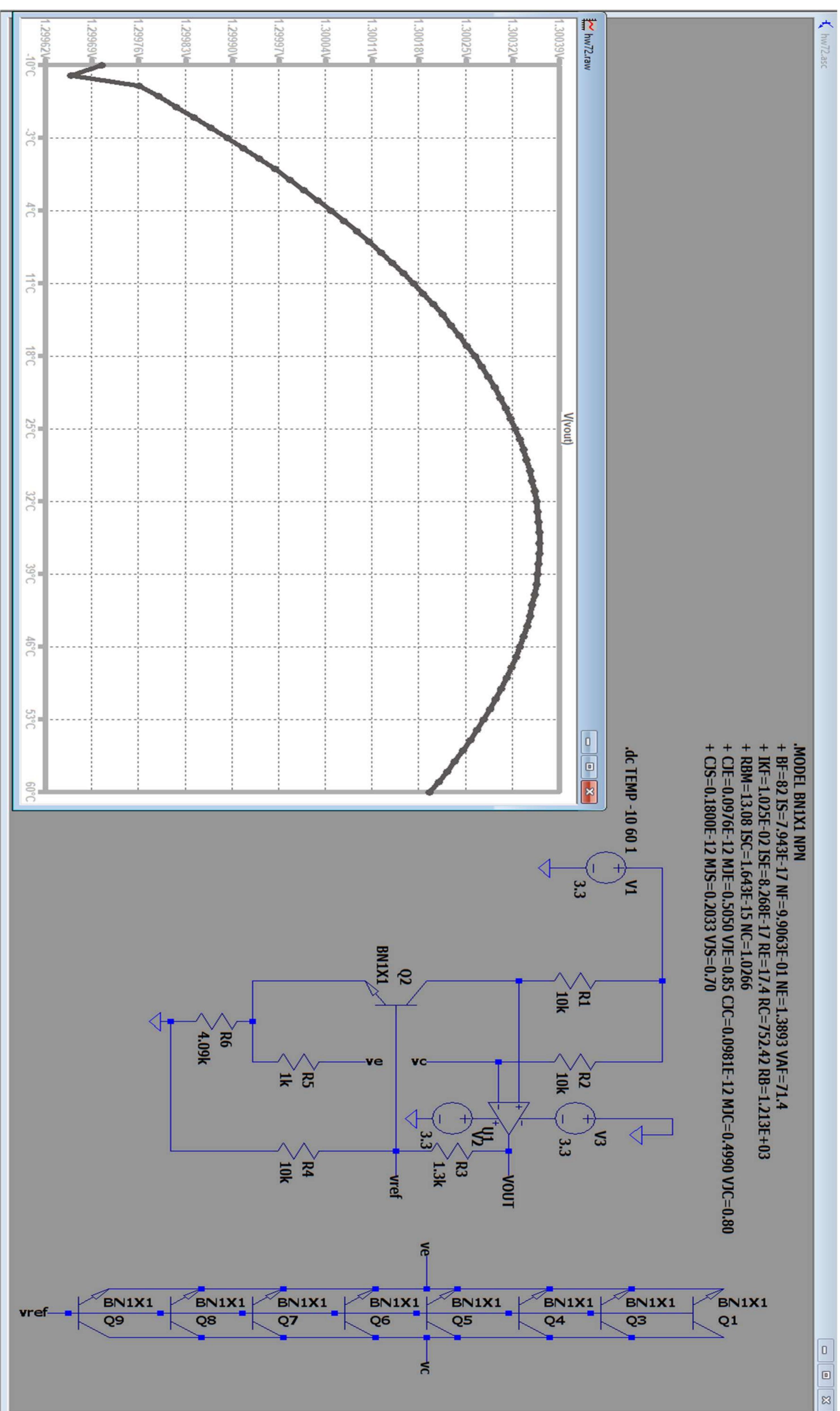After play with values, I had less than 0.1% error from -10°C to 60°C. Op-Amp is ideal.



Op-Amp with gain 50. Error is still less than 0.1%, but the output voltage is decreased.

